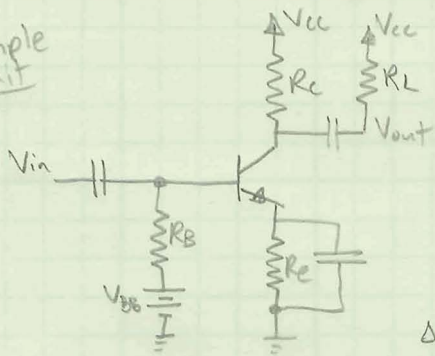



Load Line/Swing Consideration Garbage

Example Circuit



$$R_{DC} = R_C + R_E$$

$$R_{AC} = R_C || R_L$$

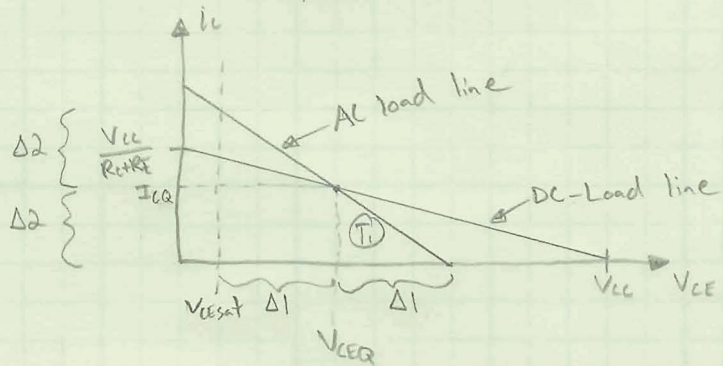


DC

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) \quad (1)$$

$$\Delta 1 = V_{CEQ} - V_{CEsat}$$

$$\Delta 2 = I_{CQ}$$

From small triangle, T_1 :

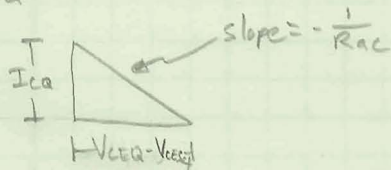

$$\therefore V_{CEQ} - V_{CEsat} = I_{CQ} \cdot R_{AC} \quad (2)$$

$$(1) + (2): V_{CC} - V_{CEsat} - I_{CQ}(R_{DC}) = I_{CQ} R_{AC}$$

$$I_{CQ}(R_{AC} + R_{DC}) = V_{CC} - V_{CEsat}$$

$$I_{CQ} = \frac{V_{CC} - V_{CEsat}}{R_{AC} + R_{DC}}$$

$$\therefore V_{CEQ} = \frac{R_{AC} V_{CC} + R_{DC} V_{CEsat}}{R_{AC} + R_{DC}}$$