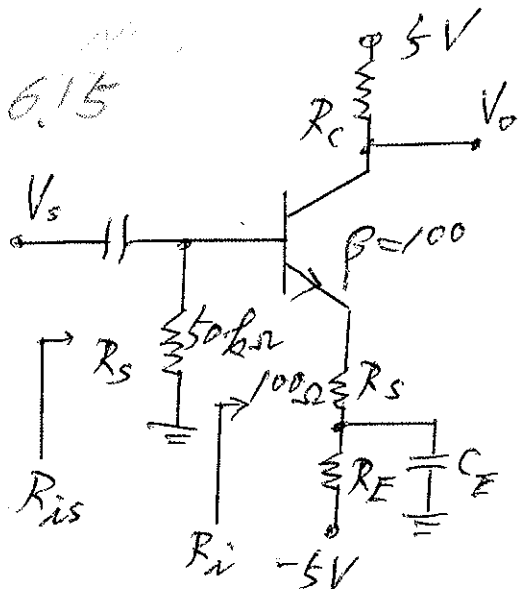


# EECE 315 Exercise # 4


D6.15



$$I_{CQ} = 0.25 \text{ mA}, \quad V_{CEQ} = 3 \text{ V}$$

dc analysis

$$I_C = \beta I_B$$

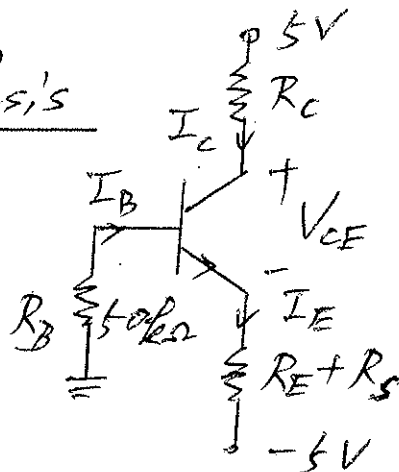

$$I_B \times R_B + 0.7 + I_E (R_E + R_S) - 5 = 0$$

$$\underline{R_E = 16.4 \text{ k}\Omega}$$

$$-5 + I_C R_C + V_{CE} + I_E (R_E + R_S) - 5 = 0$$

$$\underline{R_C = 11.3 \text{ k}\Omega}$$


$$g_m = \frac{I_{CQ}}{0.025} = 0.01 \text{ A/V}, \quad r_{\pi} = \frac{\beta}{g_m} = 10 \text{ k}\Omega$$

$$R_i = r_{\pi} + (1 + \beta) \times R_E = 20.1 \text{ k}\Omega$$


$$R_{is} = R_B \parallel R_i = \underline{\underline{14.3 \text{ k}\Omega}}$$

$$A_v = - \frac{\beta R_C}{(\beta + 1) R_E + r_{\pi}} = \underline{\underline{-56.2}}$$

6.26

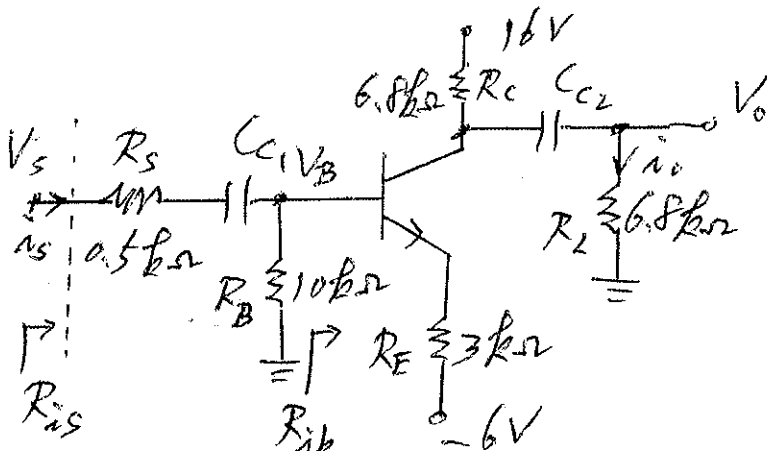

dc analysis

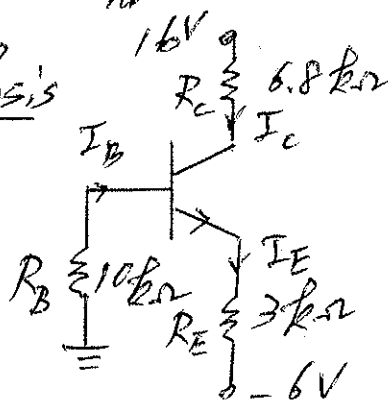

$$I_B \times R_B + 0.7 + I_E R_E - 6 = 0$$

$$\frac{I_{CQ}}{\beta} \times R_B + 0.7 + \left(\frac{I_{CQ}}{\beta} + I_{CQ}\right) R_E - 6 = 0$$

$$I_{CQ} = \underline{\underline{1.69 \text{ mA}}}$$

$$V_{CEQ} = 16 - I_{CQ} R_C - I_{EQ} \times 3 + 6$$

$$V_{CEQ} = \underline{\underline{5.39 \text{ V}}}$$

$$g_m = \frac{I_{CQ}}{0.025} = \underline{\underline{67.6 \text{ mA/V}}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \underline{\underline{1.479 \text{ k}\Omega}} \quad , \quad r_o = \infty$$

$$R_{ib} = r_{\pi} + (\beta + 1) \times R_E = \underline{\underline{304.5 \text{ k}\Omega}}$$


$$R_{is} = R_S + (R_{ib} \parallel R_B) = \underline{\underline{10.18 \text{ k}\Omega}}$$

$$\frac{V_o}{V_B} = - \frac{\beta (R_C \parallel R_L)}{(\beta + 1) R_E + r_{\pi}} = -1.117$$


$$\frac{V_o}{V_S} = \frac{V_o}{V_B} \times \frac{V_B}{V_S} \quad ; \quad \frac{V_B}{V_S} = \frac{R_{ib} \parallel R_B}{R_{ib} \parallel R_B + R_S} = 0.951$$

$$\frac{V_o}{V_S} = -1.117 \times 0.951 = \underline{\underline{-1.062}}$$
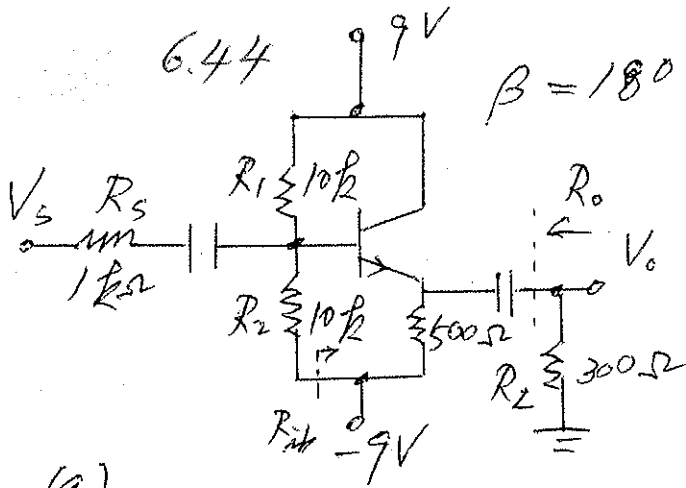
$$i_o = \frac{V_o}{R_L} \quad , \quad i_s = \frac{V_S}{R_{is}} \quad , \quad \frac{i_o}{i_s} = \frac{V_o}{V_S} \times \frac{R_{is}}{R_L} = \underline{\underline{-1.59}}$$



dc analysis

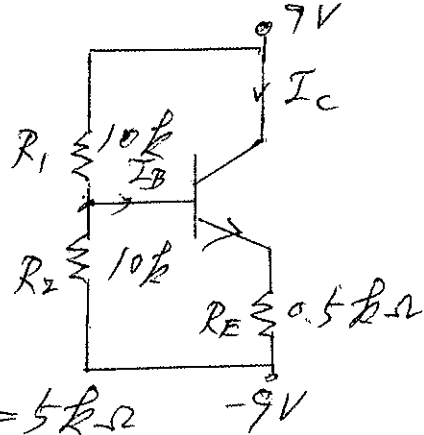


(a)

$$V_{TH} = 0 \text{ (Why)}, R_{TH} = R_1 \parallel R_2 = 5k\Omega$$

$$-V_{TH} + \frac{I_{CQ}}{\beta} \times R_{TH} + 0.7 + \left( \frac{I_{CQ}}{\beta} + I_{CQ} \right) \times 0.5 - 9 = 0$$

$$\therefore I_{CQ} = \underline{\underline{15.64 \text{ mA}}}, \quad g_m = \frac{I_{CQ}}{0.025} = 0.6256 \text{ A/V}$$
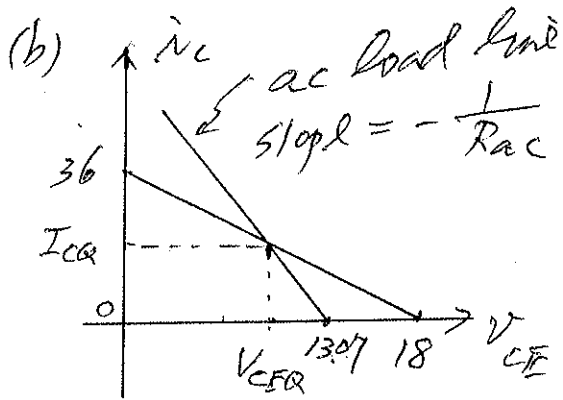
$$V_{CEQ} = 9 - (-9) - \left( I_{CQ} + \frac{I_{CQ}}{\beta} \right) \times 0.5 = \underline{\underline{10.136 \text{ V}}}$$



dc load line eq.

$$18 \approx V_{CE} + I_C R_E$$

$$R_{ac} = 500 \parallel 300 = 187.5 \Omega$$

ac load line eq.

$$V_{CE} + R_{ac} i_c = b$$


where  $b = V_{CEQ} + R_{ac} I_{CQ}$

ac load line eq.  $V_{CE} + R_{ac} i_c = V_{CEQ} + R_{ac} I_{CQ}$

(c)  $R_{ib} = r_{\pi} + (\beta + 1)(500 \parallel 300), \quad r_{\pi} = \frac{180}{g_m} = 287.7 \Omega$   
 $R_{ib} = \underline{\underline{34.2 k\Omega}}$

6.44

ac analysis

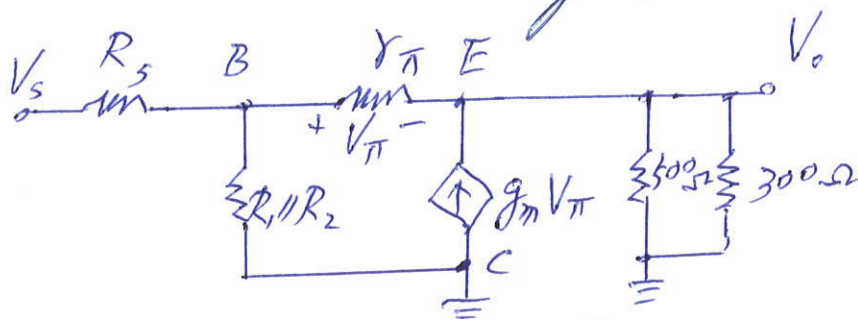

$$\frac{V_o}{500//300} - g_m V_\pi + \frac{V_o - V_B}{r_\pi} = 0 \quad ; \quad V_o - V_B = -V_\pi$$

$$\frac{V_o}{187.5} - 0.6256 V_\pi - \frac{V_\pi}{287.7} = 0 \quad , \quad \underline{V_o = 117.95 V_\pi}$$


$$\frac{V_B}{R_1//R_2} + \frac{V_\pi}{r_\pi} + \frac{V_B - V_s}{R_s} = 0 \quad ; \quad V_B = V_o + V_\pi$$

$$\left( \frac{1}{5000} + \frac{1}{1000} \right) (V_o + V_\pi) + \frac{V_\pi}{287.7} - \frac{V_s}{1000} = 0$$

$$0.0012 (V_o + 0.00848 V_o) + 0.0000295 V_o = \frac{V_s}{1000}$$

$$\therefore A_v = \frac{V_o}{V_s} = \underline{\underline{2806}}$$

(d)

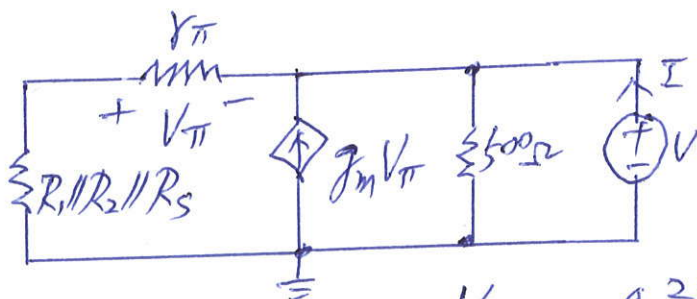Eq. circuit to determine  $R_o$ 

$$I = \frac{V}{500} - g_m V_\pi - \frac{V_\pi}{r_\pi}$$

$$V_\pi = -V \times \frac{r_\pi}{r_\pi + (R_1//R_2//R_s)}$$

$$R_1//R_2//R_s = 833.3 \Omega \quad , \quad V_\pi = -0.257 V \quad , \quad I = \frac{V}{500} - \left( g_m + \frac{1}{r_\pi} \right) V_\pi$$

$$I = \frac{V}{500} - \left( 0.6256 + \frac{1}{287.7} \right) \times (-0.257) V$$

$$\therefore R_o = \frac{V}{I} = \underline{\underline{6.11 \Omega}}$$

## 6.67 DC analysis



(a)

$$V_{CC} = 9V, R_C = 6 \text{ k}\Omega$$

$$R_E = 3 \text{ k}\Omega, R_1 = 150 \text{ k}\Omega$$

$$R_2 = 50 \text{ k}\Omega, \beta = 125$$

$$V_{BE} = 0.7V, V_A = \infty$$

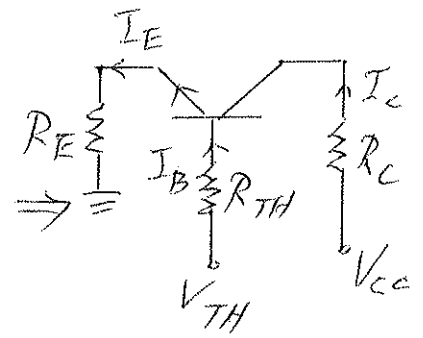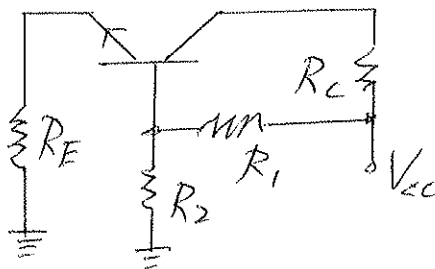

$$R_{TH} = R_1 \parallel R_2 = 37.5 \text{ k}\Omega$$

$$V_{TH} = V_{CC} \times \frac{R_2}{R_1 + R_2} = 2.25V$$

$$-V_{TH} + I_B R_{TH} + V_{BE} + I_E R_E = 0, \quad I_E = I_B + I_C = (\beta + 1)I_B$$

$$-2.25 + 37.5 \times I_B + 0.7 + 126 \times 3 \times I_B = 0, \quad I_B = 3.73 \mu A > 0$$


$$\therefore I_{CQ} = 0.466 \text{ mA}, \quad V_{CEQ} = V_{CC} - I_C R_C - I_E R_E = 4.79V$$

$$V_{BC} = V_{BE} - V_{CE} = 0.7 - 4.79 = -4.09V < 0$$
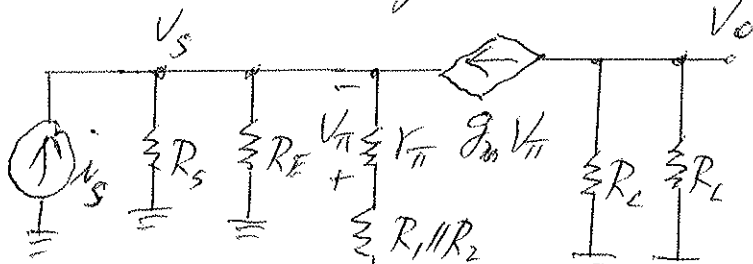
## (b) AC analysis $R_L = 4 \text{ k}\Omega$

$$g_m = \frac{I_{CQ}}{0.025} = 18.64 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = 6.706 \text{ k}\Omega$$



$$V_o = -g_m v_{\pi} \times (R_L \parallel R_C) = -44.736 V_{\pi}$$

$$V_{\pi} = -V_S \times \frac{r_{\pi}}{r_{\pi} + (R_1 \parallel R_2)}$$


$$\therefore A_v = \frac{V_o}{V_S} = 6.786 \quad (c)$$

$$i_s = \frac{V_S}{R_S} + \frac{V_S}{R_E} - g_m v_{\pi} - \frac{v_{\pi}}{r_{\pi}}$$


$$i_s = \left( \frac{1}{R_S} + \frac{1}{R_E} \right) V_S - g_m (-0.1517 V_S) - \frac{1}{r_{\pi}} (-0.1517 V_S)$$

$$i_s = \left[ \frac{1}{R_S} + \frac{1}{R_E} + 0.1517 g_m + 0.1517 \times \frac{1}{r_{\pi}} \right] V_S = 3.194 V_S$$
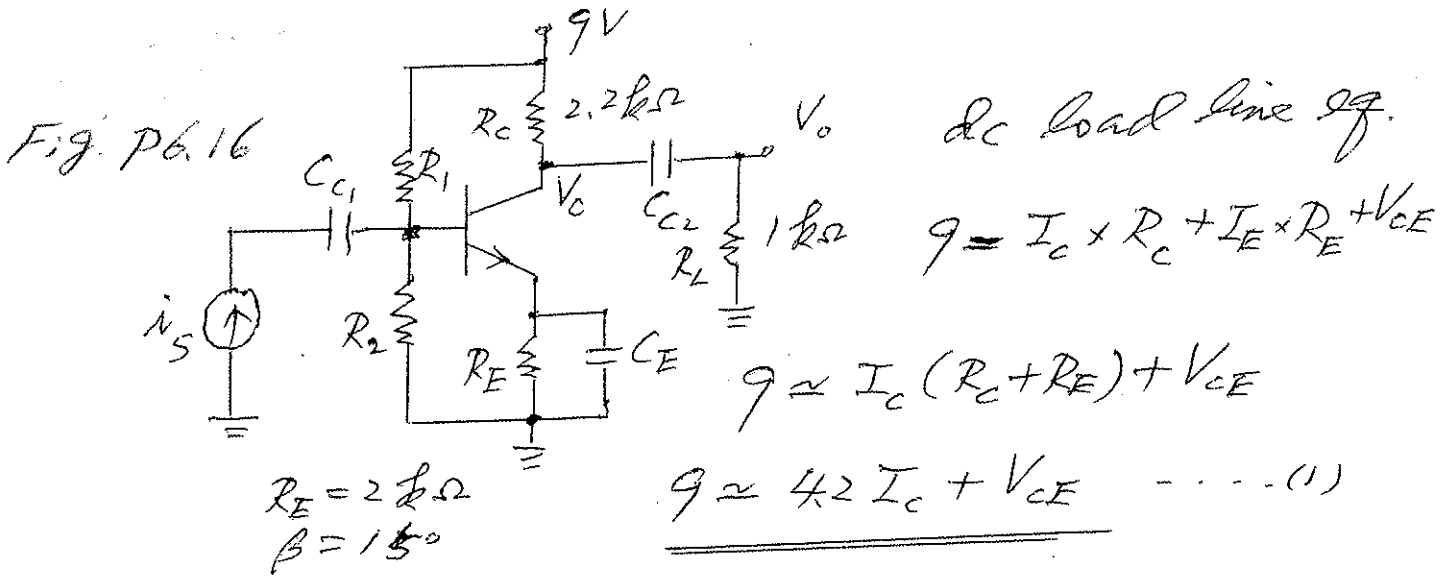
$$\frac{V_o}{i_s} = \frac{6.786 V_S}{3.194 V_S} = 2.125 \text{ k}\Omega$$


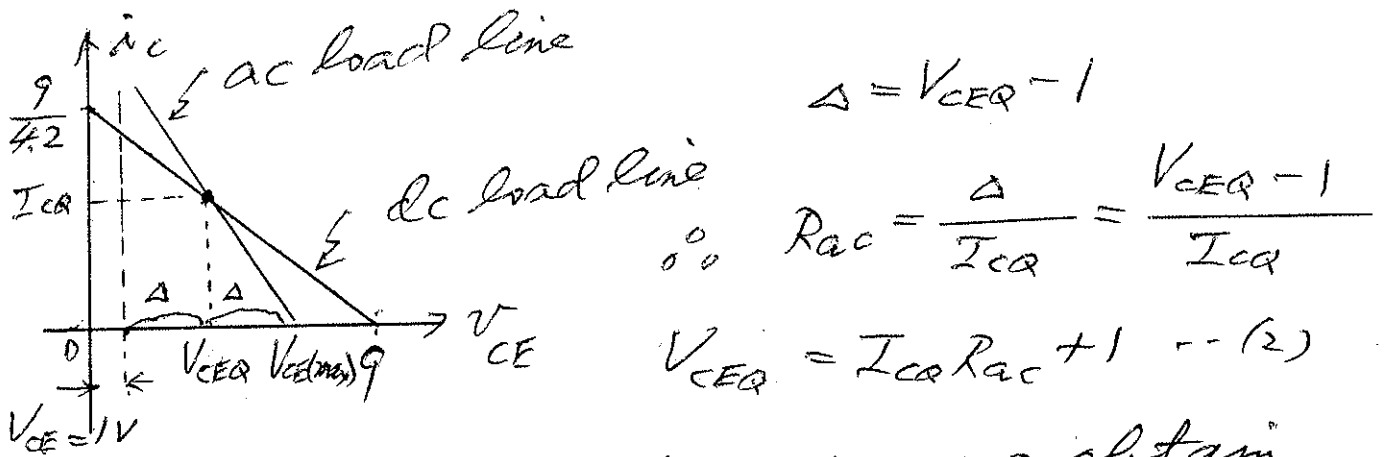
$$R_{ac} = 2.2 \parallel R_L = 0.6875 \text{ k}\Omega$$



Sub.  $V_{CEQ}$  from (2) into (1), we obtain

$$I_{CQ} = 1.64 \text{ mA} \text{ and } \underline{V_{CEQ} = 2.12 \text{ V}}$$

$$V_{CE(max)} = V_{CEQ} + \Delta = 2V_{CEQ} - 1 = 3.24 \text{ V} < 8 \text{ V}$$

Now, choose  $R_1$  and  $R_2$  to give the Q-point.

$$-9 \times \frac{R_2}{R_1 + R_2} + 0.7 + I_{BQ} \times \frac{R_1 R_2}{R_1 + R_2} + I_{EQ} R_E = 0$$

$$\text{Let } R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(1 + \beta) R_E}{10} \quad \text{or } R_E = 10 \times \frac{R_{TH}}{\beta + 1}$$

$$\underline{R_1 = 62.9 \text{ k}\Omega}, \quad \underline{R_2 = 58.1 \text{ k}\Omega}$$