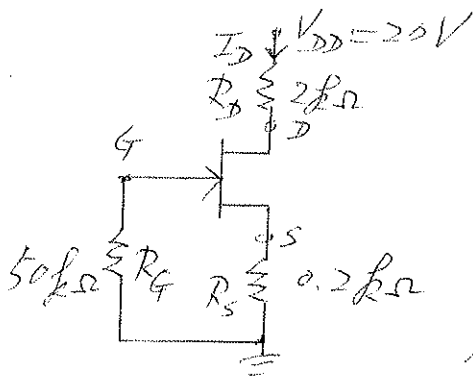


ECE 315 Exercise #5

3.63



$$I_{DSS} = 10 \text{ mA}$$

$$V_p = -5 \text{ V}$$

Assume saturation region.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = 10 \left(1 + \frac{V_{GS}}{5}\right)^2 \quad \dots (1)$$

$$20 = I_D \times 2 + V_{DS} + I_D \times 0.2 \quad \dots (2)$$

$$V_{GS} = V_G - V_S = 0 - I_D \times 0.2 = -0.2 I_D \quad \dots (3)$$

$$\text{or } \frac{I_D}{-0.2} = \frac{V_{GS}}{-5} = -5 V_{GS} \quad \dots (4)$$

Sub. (4) into (1),

$$-5 V_{GS} = 10 (1 + 0.4 V_{GS} + 0.04 V_{GS}^2)$$

$$\text{s.t. } 0.04 V_{GS}^2 + 0.9 V_{GS} + 1 = 0$$

$$V_{GS} = \frac{-0.9 \pm \sqrt{(0.9)^2 - 4 \times 0.04}}{2 \times 0.04} = -1.172 \text{ V or } -2.328 \text{ V}$$


Choose $V_{GS} > V_p$. s.t. $V_{GSR} = \underline{\underline{-1.172 \text{ V}}}$, $I_{DR} = \underline{\underline{5.86 \text{ mA}}}$

From (2), $V_{DSR} = 20 - 2.2 I_{DR} = \underline{\underline{7.11 \text{ V}}}$

$$\underline{\underline{V_{GD} = V_{GS} - V_{DS} = -8.28 \text{ V} < V_p}}$$

3.68

EE315 Exercise # 5

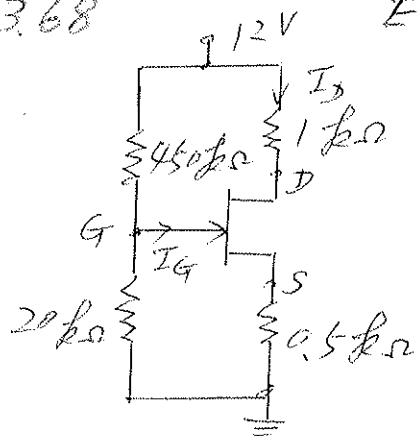

$$V_{DSR} = 5V$$

$$I_{DSS} = 10mA$$

$$I_G = 0$$

Assume saturation.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \dots \textcircled{1}$$

$$V_{GS} = V_G - V_S = 12 \times \frac{20}{20+450} - I_D \times 0.5$$

$$V_{GS} = 0.511 - 0.5 I_D \quad \dots \textcircled{2}$$

$$12 = I_D \times 1 + V_{DS} + I_D \times 0.5 = 1.5 I_D + 5 \quad \dots \textcircled{3}$$

$$\therefore I_D = \frac{12-5}{1.5} = \underline{\underline{4.67mA}}$$

$$\text{From } \textcircled{2}, V_{GS} = 0.511 - 0.5 I_D = \underline{\underline{-1.824V}}$$

Sub. I_D and V_{GS} into $\textcircled{1}$,

$$4.67 = 10 \left(1 - \frac{-1.824}{V_P}\right)^2 = 10 \left(1 + \frac{1.824}{V_P}\right)^2$$


$$\left(1 + \frac{1.824}{V_P}\right)^2 = 0.467$$

$$\therefore 1 + \frac{1.824}{V_P} = \pm \sqrt{0.467} = \pm 0.683$$

$$V_P = -1.084V \text{ or } -5.754V \quad \underline{\underline{V_P = -5.754V}}$$

$$\left[V_{GS} = V_{GS} - V_{DS} = -6.824V < V_P \right] \quad (V_{GS} > V_P)$$

369

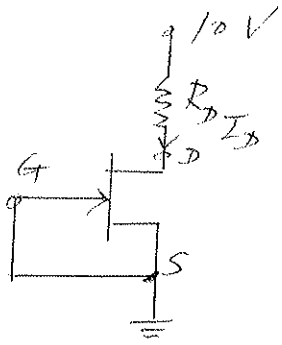

$$I_{DSS} = 4 \text{ mA}$$

$$V_p = -3 \text{ V}$$

$$V_{GS} = 0 \text{ V} > V_p$$

Assume saturation.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = I_{DSS} = 4 \text{ mA}$$


$$10 = I_D R_D + V_{DS} = I_D R_D + 3$$

$$R_D = \frac{10 - 3}{I_D} = \underline{\underline{1.75 \text{ k}\Omega}}$$

$$V_{GD} = V_{GS} - V_{DS} = 0 - 3 = -3 = V_p$$

4.77

(a) DC bias analysis

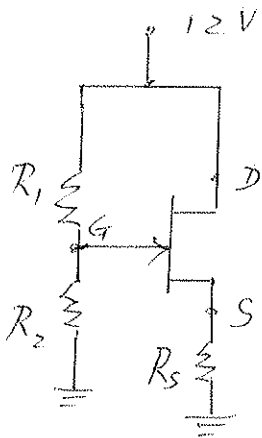

$$I_{DSS} = 10 \text{ mA}, \quad V_p = -5 \text{ V}$$

$$\lambda = 0.01 \text{ V}^{-1}$$

$$I_{DQ} = \frac{I_{DSS}}{2} = 5 \text{ mA}$$

$$V_{DSQ} = \frac{V_{DD}}{2} = 6 \text{ V}, \quad R_{in} = R_1 \parallel R_2 = 100 \text{ k}\Omega$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$1 - \frac{V_{GS}}{(-5)} = \pm \sqrt{\frac{I_{DQ}}{I_{DSS}}} = \pm \sqrt{0.5} = \pm 0.707$$

$$V_{GS} = -1.465 \text{ V or } -8.535 \text{ V} \quad \text{Choose } \underline{\underline{V_{GS} = -1.465 \text{ V} > V_p}}$$

$$V_{SA} = I_{DQ} R_S = 12 - V_{DSQ} = 6 \text{ V}, \quad \underline{\underline{R_S = \frac{6}{I_{DQ}} = 1.2 \text{ k}\Omega}}$$

D 4.77

$$V_{GS} = V_G - V_S = 12 \times \frac{R_2}{R_1 + R_2} - 6 = -1.465$$

$$\frac{R_2}{R_1 + R_2} = \frac{4.535}{12}, \text{ but } R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = R_{in} = 100 \text{ k}\Omega$$


$$\frac{R_1 R_2}{R_1 + R_2} = \frac{4.535 R_1}{12} = 100, \quad \underline{R_1 = 264.6 \text{ k}\Omega}$$

$$R_2 = \frac{4.535 R_1}{12 - 4.535} = \underline{169.8 \text{ k}\Omega}$$

$$(b) \quad g_m = \frac{2}{|V_p|} \sqrt{I_{DQ} I_{DSS}} = 2.83 \text{ mA/V}, \quad R_L = 0.5 \text{ k}\Omega$$

$$r_{ds} = r_o = \frac{1}{\lambda I_{DQ}} = 20 \text{ k}\Omega$$

$$V_G = V_i, \quad V_S = V_o$$

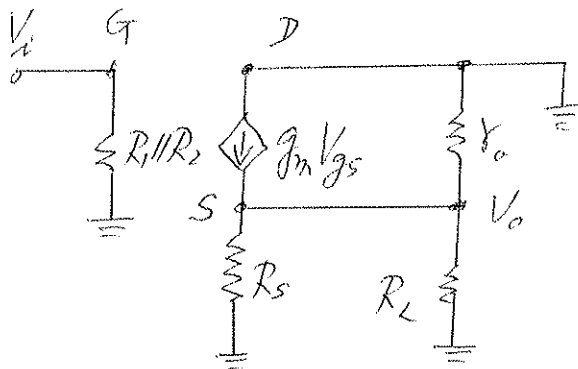

$$\frac{V_o}{R_s} + \frac{V_o}{R_L} + \frac{V_o}{r_o} - g_m V_{GS} = 0$$

$$\frac{V_o}{(R_s \parallel R_L \parallel r_o)} - g_m (V_i - V_o) = 0$$

$$R_s \parallel R_L \parallel r_o = 0.347 \text{ k}\Omega$$

$$\left(\frac{1}{0.347} + 2.83 \right) V_o = 2.83 V_i, \quad \underline{A_V = \frac{V_o}{V_i} = 0.495}$$


Output resistance

$$V_G = 0, \quad V_S = V$$


$$I + g_m V_{GS} = \frac{V}{R_s} + \frac{V}{r_o} = \frac{V}{R_s \parallel r_o} = \frac{V}{1.132}$$

$$I + 2.83 \times (0 - V) = \frac{V}{1.132}$$
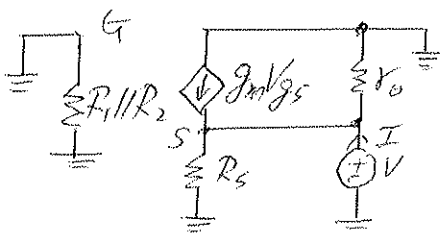
$$\underline{R_o = \frac{V}{I} = 0.269 \text{ k}\Omega}$$



4.78

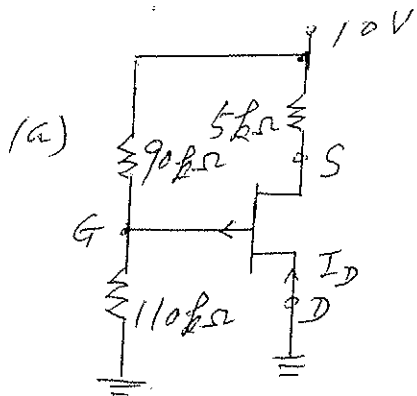

$$I_{DSS} = -2 \text{ mA}, V_p = 1.75 \text{ V}$$

$$\lambda = 0 \quad (r_o = \infty)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = -2 \left(1 - \frac{V_{GS}}{1.75}\right)^2 < 0 \quad \text{--- (1)}$$

$$V_{GS} = V_G - V_S = 10 \times \frac{110}{110 + 90} - (10 + I_D \times 5)$$

$$V_{GS} = 5.5 - 10 - 5 I_D \quad \text{or} \quad I_D = \frac{-4.5 - V_{GS}}{5} \quad \text{--- (2)}$$

Sub. (2) into (1),

$$\frac{-4.5 - V_{GS}}{5} = -2 \left(1 - \frac{V_{GS}}{1.75}\right)^2$$


$$0.3265 V_{GS}^2 - 1.243 V_{GS} + 0.55 = 0$$

$$V_{GS} = 3.296 \text{ V} \quad \text{or} \quad 0.511 \text{ V}$$

Choose $V_{GS} = 0.511 \text{ V} < 1.75 \text{ V}$

$$I_{DA} = \frac{-4.5 - V_{GS}}{5} = \underline{\underline{-1 \text{ mA}}}$$
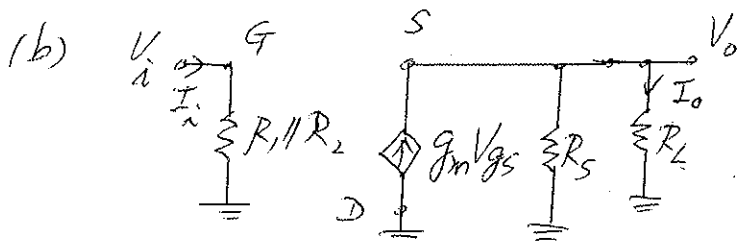
$$V_{SDA} = 10 + 5 \times I_{DA} = \underline{\underline{5 \text{ V}}}$$



$$V_o = g_m V_{gs} (R_s \parallel R_L)$$

$$g_m = \frac{2}{|V_p|} \sqrt{I_{DA} I_{DSS}} = 1.616 \text{ mA/V}$$

$$V_{gs} = V_g - V_s = V_i - V_o$$


$$A_v = \frac{V_o}{V_i} = \frac{g_m (R_s \parallel R_L)}{1 + g_m (R_s \parallel R_L)} = \underline{\underline{0.843}}$$

4.78

$$(b) \quad I_o = \frac{V_o}{R_L}, \quad I_i = \frac{V_i}{(R_1 \parallel R_2)}$$

$$\therefore A_i = \frac{I_o}{I_i} = \frac{V_o}{V_i} \times \frac{R_1 \parallel R_2}{R_L} = 0.843 \times \frac{49.5}{10}$$

$$A_i = \underline{\underline{4.17}}$$

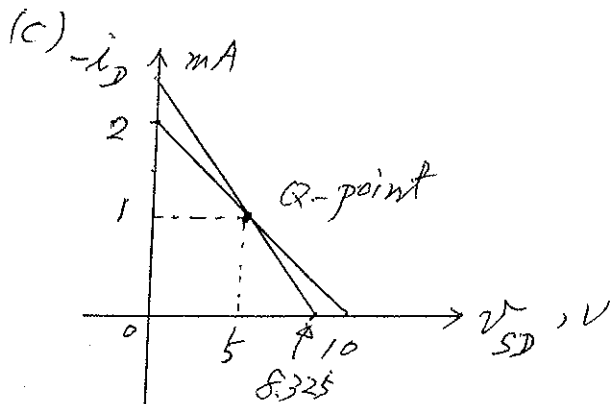

dc load line eq.

$$10 = -5 I_D + V_{SD}$$

$$R_{ac} = R_S \parallel R_L = 3.33 \text{ k}\Omega$$

ac load line eq.

$$-i_D = -\frac{1}{R_{ac}} v_{SD} + b$$

(a) the Q-point, $i_D = -1 \text{ mA}$, $v_{SD} = 5 \text{ V}$

$$\therefore b = 2.5 \text{ mA}$$

$$\therefore -i_D = -\frac{1}{R_{ac}} v_{SD} + 2.5$$

Let $i_D = 0$, $v_{SD} = 8.325 \text{ V}$

4.78 (c)

Since $v_{SD}(ac) = v_o$, then $v_{o,max} = 8.325 V$.

$$v_{o,min} = v_{SD,min} = V_p - V_{GS} \quad \left(\begin{array}{l} \text{Triode region} \\ V_{GD} = V_p = V_{GS} - V_{DS} \end{array} \right)$$

where $V_{GS} \neq V_{GSQ}$

$$\begin{cases} v_{SD,min} = 10 - i_{SD,max} \times 5 = V_p - V_{GS} \\ i_{SD,max} = |I_{DSS}| \left(1 - \frac{V_{GS}}{V_p} \right)^2 \end{cases}$$

$$v_{SD,max} = \frac{10 - V_p + V_{GS}}{5} = \frac{10 - 1.75 + V_{GS}}{5} = \frac{8.25 + V_{GS}}{5}$$

$$\therefore \frac{8.25 + V_{GS}}{5} = |I_{DSS}| \left(1 - \frac{V_{GS}}{V_p} \right)^2 = 2 \left(1 - \frac{V_{GS}}{1.75} \right)^2$$

$$8.25 + V_{GS} = 10 \left(1 - \frac{2V_{GS}}{1.75} + \frac{V_{GS}^2}{(1.75)^2} \right)$$

$$3.265 V_{GS}^2 - 12.43 V_{GS} + 1.75 = 0$$

$$V_{GS} = \begin{cases} 3.65 V \\ 0.148 V \end{cases} \quad (V_{GS} < V_p)$$

$$\therefore v_{o,min} = V_p - 0.148 = 1.602 V$$

$$\Delta v_{o,up} = 8.325 - 5 = 3.325 V$$

$$\Delta v_{o,down} = 5 - 1.602 = 3.398 V$$

$$\therefore v_{o,p.p,max} = 2 \times 3.325 = \underline{\underline{6.65 V}}$$