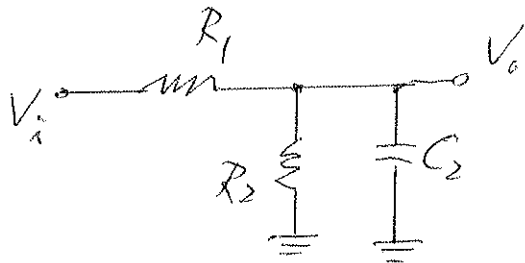



# EECE-315 Exercise # 6

7.3



$R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$   
 $C_2 = 10 \text{ }\mu\text{F}$

(a)

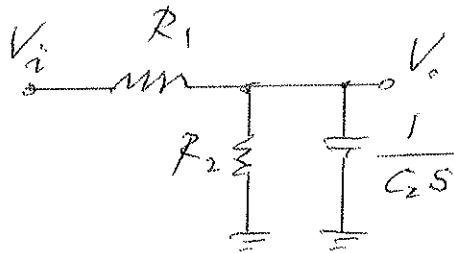

$$R_2 \parallel \frac{1}{C_2 s} = \frac{R_2 \times \frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}} = \frac{R_2}{R_2 C_2 s + 1}$$

$$V_o = V_i \times \frac{R_2 C_2 s + 1}{R_1 + \frac{R_2}{R_2 C_2 s + 1}} = V_i \times \frac{R_2}{R_1 R_2 C_2 s + R_1 + R_2}$$

$$\therefore H(s) = T(s) = \frac{V_o}{V_i} = \frac{R_2}{R_1 R_2 C_2 s + R_1 + R_2} = \frac{20}{25s + 30} = \frac{10}{s + 15}$$

(b)  $\tau = (R_1 \parallel R_2) \times C_2 = \left( \frac{R_1 R_2}{R_1 + R_2} \right) \times C_2 = \frac{1}{15} = \underline{\underline{66.7 \text{ msec}}}$


(c)  $H(j\omega) = H(j2\pi f) = \frac{10}{j2\pi f + 15} = \frac{10}{15(1 + j\frac{2\pi f}{15})}$

$H(j2\pi f) = \frac{\frac{2}{3}}{1 + j\frac{f}{f_1}}$  where  $f_1 = \frac{15}{2\pi} = 2.387 \text{ Hz}$


Corner freq. = 2.387 Hz

(d)  $|H(j2\pi f)| = \frac{\frac{2}{3}}{\sqrt{1 + (\frac{f}{f_1})^2}}$ ;  $|H(j2\pi f)|_{f=0} = \frac{2}{3}$   
 $|H(j2\pi f)|_{f=\infty} = 0$

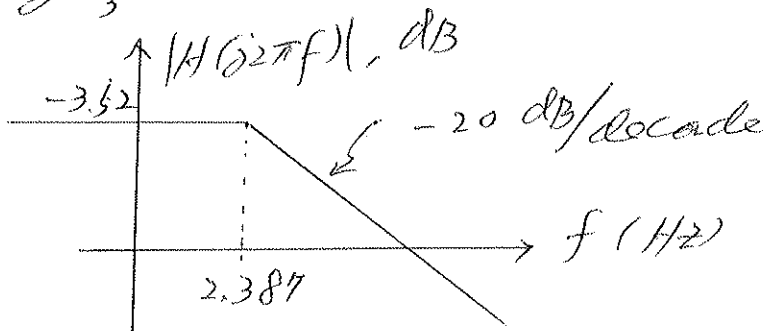$20 \log(\frac{2}{3}) = -3.52 \text{ dB}$



7.5

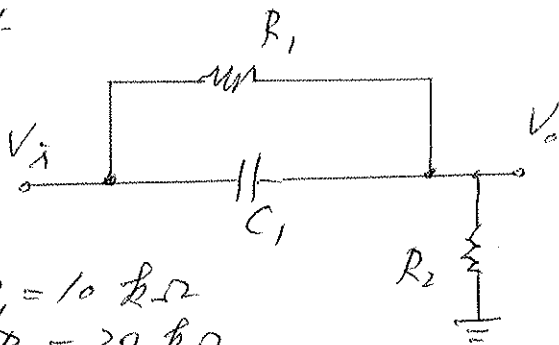

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 20 \text{ k}\Omega$$

$$C_1 = 10 \text{ }\mu\text{F}$$

$$R_1 \parallel \frac{1}{C_1 s} = \frac{R_1 \times \frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} = \frac{R_1}{R_1 C_1 s + 1}$$

$$V_o = V_i \times \frac{R_2}{R_2 + \left( \frac{R_1}{R_1 C_1 s + 1} \right)}$$

$$H(s) = \frac{V_o}{V_i} = \frac{R_2 (R_1 C_1 s + 1)}{R_2 (R_1 C_1 s + 1) + R_1} = \frac{R_1 R_2 C_1 s + R_2}{R_1 R_2 C_1 s + (R_1 + R_2)}$$

$$H(j\omega) = \frac{j\omega R_1 R_2 C_1 + R_2}{j\omega R_1 R_2 C_1 + (R_1 + R_2)}$$

$$(a) \quad H(j\omega) \Big|_{\omega=0} = \frac{R_2}{R_1 + R_2} = \underline{\underline{\frac{2}{3}}}$$

$$(b) \quad H(j\omega) \Big|_{\omega=\infty} = \underline{\underline{1}}$$

$$(c) \quad H(s) = T(s) = \frac{2s + 20}{2s + 30} = \underline{\underline{\frac{s + 10}{s + 15}}}$$


$$(d) \quad T(s) = \frac{10 \left( 1 + \frac{s}{10} \right)}{15 \left( 1 + \frac{s}{15} \right)} = \underline{\underline{\frac{2}{3} \times \frac{1 + \frac{1}{10}s}{1 + \frac{1}{15}s}}}$$

$$K = \frac{2}{3} \quad (= H(j\omega) \Big|_{\omega=0})$$

$$\tau_A = \frac{1}{10} = 0.1 \text{ sec}$$

$$\tau_B = \frac{1}{15} = 66.7 \text{ msec}$$

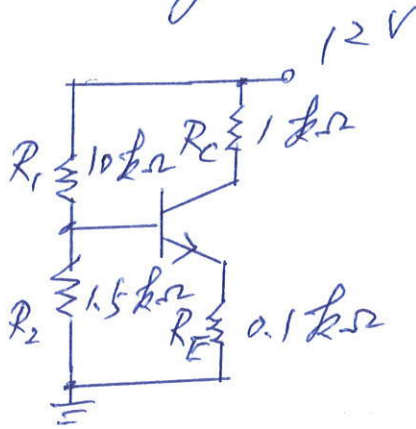7.17 dc analysis to determine  $I_{CQ}$ .




$$-12 \times \frac{1.5}{10+1.5} + \frac{I_{CQ} \times R_{TH} + 0.7}{\beta} + \left(\frac{I_{CQ}}{\beta} + I_{CQ}\right) \times R_E = 0$$

$$R_{TH} = R_1 \parallel R_2 = 1.3 \text{ k}\Omega$$

$$I_{CQ} = \underline{7.59 \text{ mA}}$$

$$g_m = \frac{I_{CQ}}{0.025} = \underline{303.6 \text{ mA/V}}, \quad r_{\pi} = \frac{\beta}{g_m} = \underline{329.4 \Omega}$$

ac low-freq. analysis

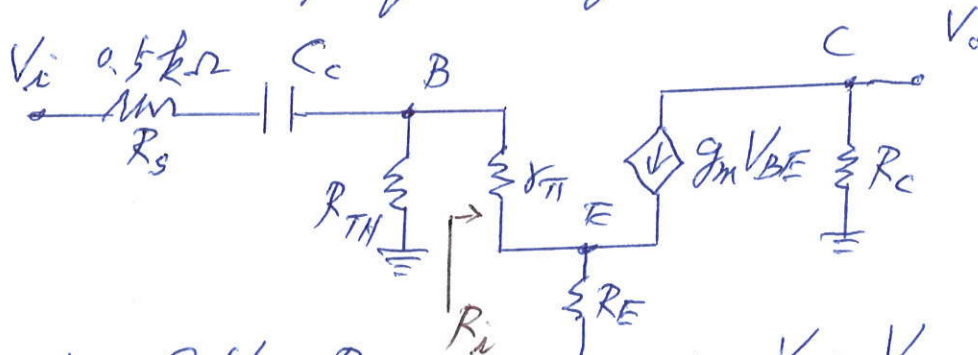

$$V_o = -g_m V_{BE} \times R_C$$

$$V_o = -303.6 V_{BE} \dots \textcircled{1}$$

$$\frac{V_B}{R_{TH}} + \frac{V_{BE}}{r_{\pi}} + \frac{V_B - V_i}{R_S + \frac{1}{C_S}} = 0$$

$$\left(\frac{1}{R_{TH}} + \frac{1}{R_S + \frac{1}{C_S}}\right) V_B + \frac{V_{BE}}{r_{\pi}} = \frac{V_i}{R_S + \frac{1}{C_S}} \dots \textcircled{2}$$

$$\frac{V_E - V_B}{r_{\pi}} + \frac{V_E}{R_E} - g_m V_{BE} = 0$$

$$-\frac{V_{BE}}{r_{\pi}} - g_m V_{BE} + \frac{V_E}{R_E} = 0$$

$$\therefore V_E = \left(\frac{1}{r_{\pi}} + g_m\right) R_E V_{BE}$$

$$V_B = V_{BE} + V_E$$

$$V_B = \left(1 + \frac{R_E}{r_{\pi}} + g_m R_E\right) V_{BE} \dots \textcircled{3}$$

$$V_B = 31.66 V_{BE}$$

2.17 Combining eqs ①, ② and ③, we obtain

$$A_v = H(s) = \frac{V_o}{V_i} = - \frac{11080 C_c s}{1 + 1655.5 C_c s} \quad \begin{array}{l} A_{v(MB)} = - \frac{11080}{1655.5} \\ = -6.69 \end{array}$$

$$f_L = \frac{1}{2\pi \times (1655.5 \times C_c)} = \underline{\underline{961.4 \text{ Hz}}}$$

Another method

Since  $C_c$  is the only capacitor, we can determine the  $f_L$  by the time constant due to  $C_c$ .

$$R_i = r_{\pi} + (1 + \beta) R_E = 10.43 \text{ k}\Omega$$

$$R_S + (R_{TH} \parallel R_i) = 1.66 \text{ k}\Omega$$



$$\therefore f_L = \frac{1}{2\pi \times 1.66 \times 10^3 \times 0.1 \times 10^{-6}} = \underline{\underline{958.8 \text{ Hz}}}$$

$$A_{v, MB} = - \frac{g_m R_c}{1 + g_m R_E} \times \frac{R_i \parallel R_{TH}}{R_S + (R_{TH} \parallel R_i)}$$

$$A_{v, MB} = \underline{\underline{-6.77}}$$

7.21

(a) dc analysis

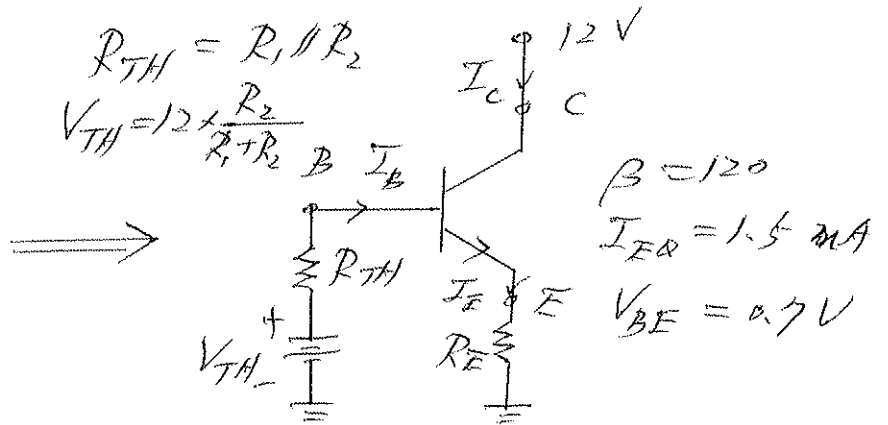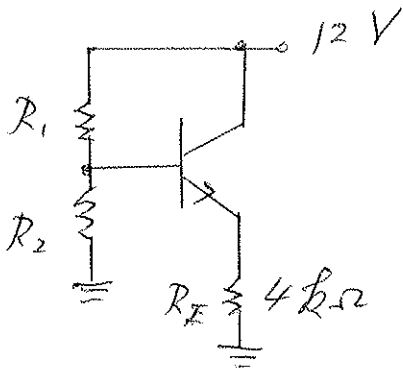

Let  $(\beta + 1)R_E = 10 R_{TH}$ ,  $\therefore R_{TH} = \frac{121}{10} \times 4 = 48.4 \text{ k}\Omega$

$$-V_{TH} + I_B \times R_{TH} + V_{BE} + I_E \times R_E = 0$$

$$-12 \times \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_1} + \frac{I_E}{\beta + 1} \times R_{TH} + 0.7 + R_E I_E = 0$$

$$-12 \times \frac{R_{TH}}{R_1} + \left( \frac{R_{TH}}{\beta + 1} + R_E \right) \times I_E + 0.7 = 0$$

$$\therefore \frac{(48.4 + 4) \times 1.5 + 0.7}{121} = \frac{(12 \times 48.4)}{R_1}$$


$$R_1 = \frac{580.8}{7.3} = 79.56 \text{ k}\Omega, \quad \frac{R_1 R_2}{R_1 + R_2} = R_{TH}$$

$$R_2 = \frac{R_1 \times R_{TH}}{R_1 - R_{TH}} = 123.6 \text{ k}\Omega$$

(b)  $g_m = \frac{I_{CQ}}{0.025} = \frac{I_{EQ} \times \beta}{0.025(\beta + 1)} = 59.5 \text{ mA/V}$

$$r_{\pi} = \frac{\beta}{g_m} = 2.017 \text{ k}\Omega, \quad r_o = \frac{V_A}{I_{CQ}} = \frac{50}{I_{EQ} \times \frac{\beta}{\beta + 1}} = 33.61 \text{ k}\Omega$$

ac equivalent circuit (midband)

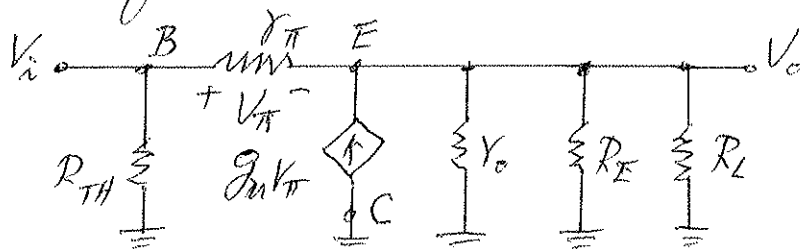


$$r_o \parallel R_E \parallel R_L = 1.888 \text{ k}\Omega$$

$$7.21 (b) \quad \frac{V_o}{1.888} - g_m V_{\pi} - \frac{V_{\pi}}{r_{\pi}} = 0; \quad V_{\pi} = V_i - V_o$$

$$\therefore \frac{V_o}{1.888} - (g_m + \frac{1}{r_{\pi}}) \times (V_i - V_o) = 0$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m + \frac{1}{r_{\pi}}}{\frac{1}{1.888} + (g_m + \frac{1}{r_{\pi}})} = 991$$

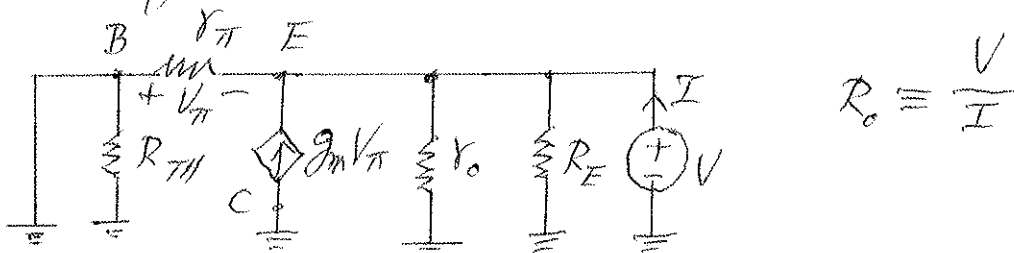(c) equivalent circuit to determine  $R_o$




$$I = \frac{V}{R_E} + \frac{V}{R_o} - g_m V_{\pi} - \frac{V_{\pi}}{r_{\pi}}; \quad V_{\pi} = 0 - V = -V$$

$$\therefore I = \left( \frac{1}{R_E} + \frac{1}{R_o} + g_m + \frac{1}{r_{\pi}} \right) V = 60.28 V$$

$$R_o = \frac{V}{I} = 0.01659 \text{ k}\Omega = \underline{\underline{16.59 \Omega}}$$

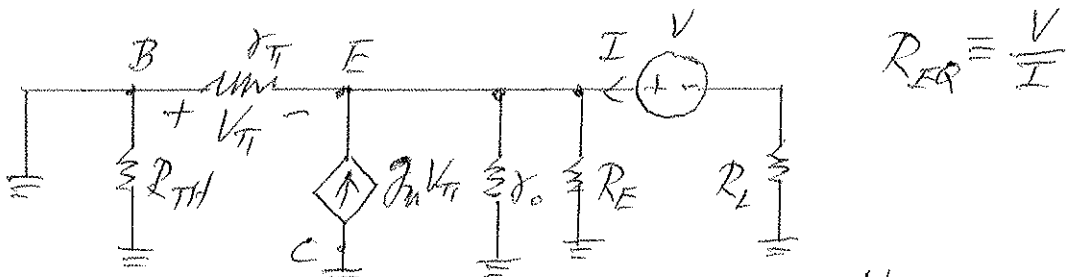(d) Short-circuit time constant for  $C_2$



$$-I + \frac{V - IR_L}{R_E} + \frac{V - IR_L}{R_o} - g_m V_{\pi} - \frac{V_{\pi}}{r_{\pi}} = 0; \quad V_{\pi} = 0 - (V - IR_L) = IR_L - V$$

$$\left( 1 + \frac{R_L}{R_E} + \frac{R_L}{R_o} \right) I + \left( \frac{1}{R_E} + \frac{1}{R_o} \right) V - (g_m + \frac{1}{r_{\pi}}) (IR_L - V) = 0$$

$$\therefore R_{EQ} = \frac{V}{I} = \frac{1 + \frac{R_L}{R_E} + \frac{R_L}{R_o} + (g_m + \frac{1}{r_{\pi}}) R_L}{\frac{1}{R_E} + \frac{1}{R_o} + g_m + \frac{1}{r_{\pi}}} = \underline{\underline{4.017 \text{ k}\Omega}}$$

$$\tau = R_{EQ} C_2 = \underline{\underline{8.034 \text{ msec}}} \quad f_2 = \frac{1}{2\pi\tau} = \underline{\underline{19.8 \text{ Hz}}}$$

# D7.30 dc analysis


$$-5 \times \frac{R_2}{R_1 + R_2} + 0.7 + \frac{R_1 R_2}{R_1 + R_2} \times I_B + R_E I_E = 0$$

$$-2.5 + 0.7 + 0.6 \times \frac{I_C}{100} + \frac{101}{100} I_C \times 0.5 = 0$$

$$\therefore \underline{I_C = 31.9 \text{ mA}}$$

$$g_m = \frac{I_C}{0.025} = 1.276 \text{ A/V} \quad r_{\pi} = \frac{\beta}{g_m} = 78.4 \Omega$$

## Short-Circuit Time Constant for $C_2$

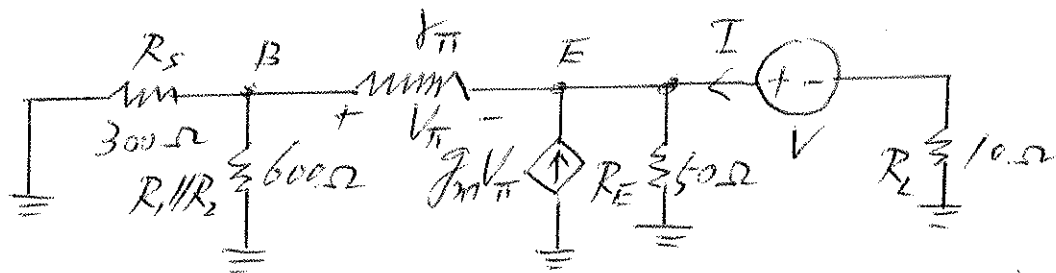

$$600 // 300 = 200 \Omega \quad V_E = V - IR_2 = V - 10I \quad \dots \textcircled{1}$$

$$\frac{V}{50} - I - g_m V_{\pi} + \frac{V_E}{78.4 + 200} = 0 \quad \dots \textcircled{2}$$


$$V_{\pi} = -V_E \times \frac{78.4}{78.4 + 200} = -0.282(V - 10I) \quad \dots \textcircled{3}$$

Combining eqs.  $\textcircled{1}$ ,  $\textcircled{2}$  and  $\textcircled{3}$ , we obtain

$$\frac{V}{I} = 11.31 \Omega, \quad \frac{1}{11.31 \times C_2} = 2\pi \times 25$$

$$\therefore \underline{C_2 = 562 \mu\text{F}}$$

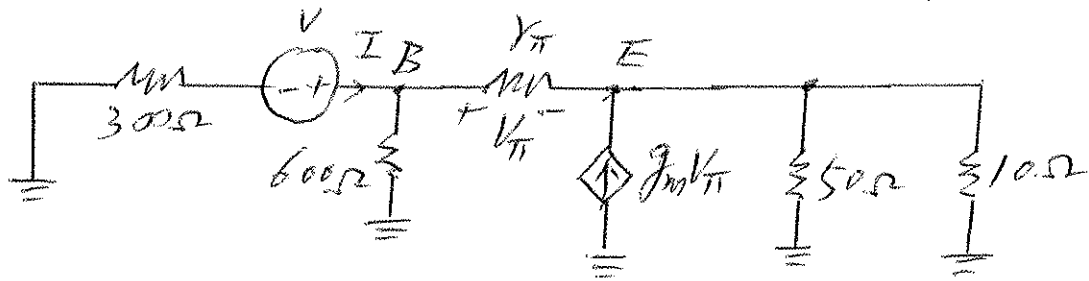D7.30 Short-circuit Time constant for  $C_1$



$$50 \parallel 10 = 8.33 \Omega$$

$$V_B = V - 300I \quad \text{--- (1)}, \quad V_\pi = V_B - V_E \quad \text{--- (2)}$$

$$\frac{V_B}{600} - I + \frac{V_\pi}{r_\pi} = 0 \quad \text{--- (3)}$$

$$\frac{V_E}{50 \parallel 10} - g_m V_\pi - \frac{V_\pi}{r_\pi} = 0 \quad \text{--- (4)}$$

Combining eqs. (1), (2), (3) and (4), we obtain

$$\frac{V}{I} = \underline{\underline{663 \Omega}}$$

$$663 \times C_1 = 100 \times 11.31 \times C_2$$

$$\therefore C_1 = \frac{100 \times 11.31 \times 562}{663} = \underline{\underline{959 \mu\text{F}}}$$

# 6.76 dc analysis

(a)

$$-12 \times \frac{12.7}{12.7+67.3} + \frac{12.7 \times 67.3}{12.7+67.3} \times \frac{I_{CQ1}}{120} + 0.7 + \frac{121}{120} I_{CQ1} \times 2 = 0$$

$$\therefore I_{CQ1} = 0.572 \text{ mA}$$

$$-12 \times \frac{45}{45+15} + \frac{45 \times 15}{45+15} \times \frac{I_{CQ2}}{120} + 0.7 + \frac{121}{120} I_{CQ2} \times 1.6 = 0$$


$$I_{CQ2} = 4.86 \text{ mA}$$

$$g_{m1} = \frac{I_{CQ1}}{0.025} = 22.88 \text{ mA/V}, \quad Y_{\pi 1} = \frac{120}{g_{m1}} = 5.245 \text{ k}\Omega$$

$$g_{m2} = \frac{I_{CQ2}}{0.025} = 194.4 \text{ mA/V}, \quad Y_{\pi 2} = \frac{120}{g_{m2}} = 0.6173 \text{ k}\Omega$$

$$Y_{o1} = Y_{o2} = \infty \quad (V_A = \infty)$$

(c)

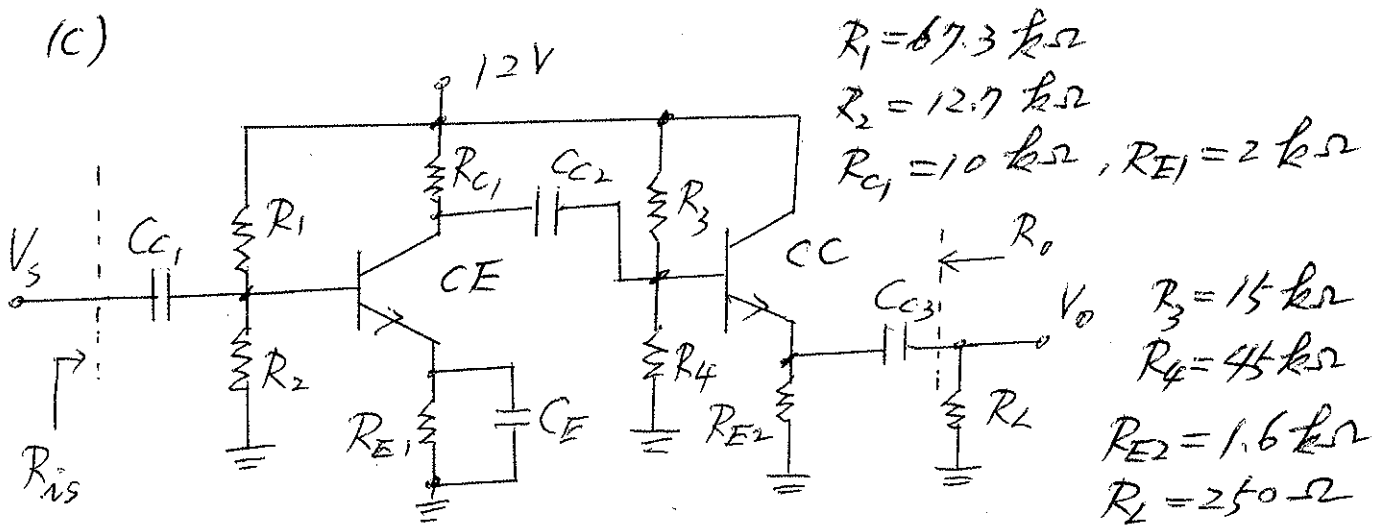

$$\frac{V_o}{V_s} = \frac{V_o}{V_{b2}} \times \frac{V_{b2}}{V_s}$$


6.76

$$\frac{V_o}{V_{b2}} = \frac{g_{m2} + \frac{1}{r_{\pi 2}}}{g_{m2} + \frac{1}{r_{\pi 2}} + \frac{1}{R_{E2} \parallel R_L}} = \underline{\underline{0.999}}$$

$$\frac{V_{b2}}{V_s} = -g_{m1} \times \left\{ R_{C1} \parallel R_3 \parallel R_4 \parallel \left[ r_{\pi 2} + (1 + \beta_2)(R_{E2} \parallel R_L) \right] \right\} = -101$$

$$\frac{V_o}{V_s} = \frac{V_o}{V_{b2}} \times \frac{V_{b2}}{V_s} = \underline{\underline{-101}}$$
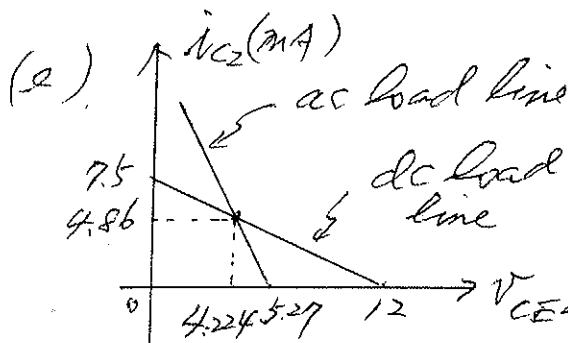
$$(d) R_{is} = R_1 \parallel R_2 \parallel Y_{\pi 1} = \underline{\underline{3.52 \text{ k}\Omega}}, R_o = \frac{(R_3 \parallel R_4 \parallel R_{C1}) + r_{\pi 2}}{1 + \beta_2} = \underline{\underline{48.9 \Omega}}$$



dc load line eq.

$$12 = V_{CE2} + I_{C2} R_{E2}$$

$$I_{CQ2} = 4.86 \text{ mA}, V_{CEQ2} = 4.224 \text{ V}$$

$$R_{ac} = 1.5 \parallel 0.25 = 0.216 \text{ k}\Omega$$

ac load line eq.  $i_{C2} = -\frac{1}{0.216} V_{CE2} + b$

$$0 = I_{CQ2} + \frac{V_{CEQ2}}{0.216} = 24.41 \text{ mA}$$

$$i_{C2} = -\frac{V_{CE2}}{0.216} + 24.41$$

When  $i_{C2} = 0$ ,  $V_{CE2} = 24.41 \times 0.216 = 5.27 \text{ V}$

$$V_{E2} = 12 - 5.27 = 6.73 \text{ V}, \frac{6.73}{R_{E2}} = 4.21 \text{ mA}$$

$$V_{out} = -4.21 \times R_L = \underline{\underline{-1.05 \text{ V}}} \quad (V_{out, min})$$


When  $V_{CE2} = 0.2 \text{ V}$  (saturation),  $V_{E2} = 12 - 0.2 = 11.8 \text{ V}$

$$i_{C2} = -\frac{0.2}{0.216} + 24.41 = 23.48 \text{ mA}, V_{out} = \left( 23.48 - \frac{11.8}{R_{E2}} \right) \times R_L$$

$$\therefore V_{out} = \underline{\underline{4.03 \text{ V}}} \quad (V_{out, max}), \quad \underline{\underline{V_{out, dc} = 0 \text{ V}}}$$

$$\Delta V_o, peak = \underline{\underline{1.05 \text{ V}}}$$

6.78 (a)

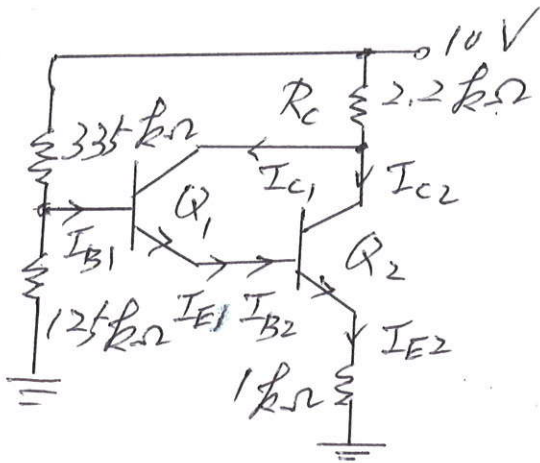

Assume  $Q_1$  and  $Q_2$  are biased in active region.

$$V_{BE1} = V_{BE2} = 0.7 \text{ V}$$

$$\beta_1 = \beta_2 = 100$$

$$-10 \times \frac{125}{125+335} + I_{B1} \times \frac{125 \times 335}{125+335} + V_{BE1} + V_{BE2} + I_{E2} \times 1 = 0$$

$$-2.72 + 91 I_{B1} + 0.7 + 0.7 + I_{C2} + I_{B2} = 0$$

$$-2.72 + 91 I_{B1} + 1.4 + 101 I_{B2} = 0 \quad \dots \textcircled{1}$$

$$I_{B2} = I_{E1} = I_{C1} + I_{B1} = 101 I_{B1} \quad \dots \textcircled{2}$$

Combining eqs.  $\textcircled{1}$  and  $\textcircled{2}$ , we obtain

$$-2.72 + 1.4 + 91 I_{B1} + 101 \times 101 I_{B1} = 0$$

$$\therefore I_{B1} = 12.8 \mu\text{A}, \quad \underline{I_{C1} = 1.28 \text{ mA}}, \quad g_{m1} = 51.2 \text{ mA/V}$$

$$I_{B2} = 12.9 \mu\text{A}, \quad \underline{I_{C2} = 1.29 \text{ mA}}, \quad g_{m2} = 51.6 \text{ mA/V}$$

$$V_{B1} = 0.7 + 0.7 + I_{E2} \times 1 \approx 2.69 \text{ V}, \quad V_{C1} = V_{C2} = 10 - 2.2(I_{C1} + I_{C2})$$


$$V_{C1} = V_{C2} = 7.13 \text{ V}$$

$$V_{BC1} = -4.44 \text{ V}$$

$$V_{B2} = 0.7 + I_{E2} \times 1 \approx 1.99 \text{ V}$$


$$V_{BC2} = -5.14 \text{ V}$$

(b) ac equivalent circuit

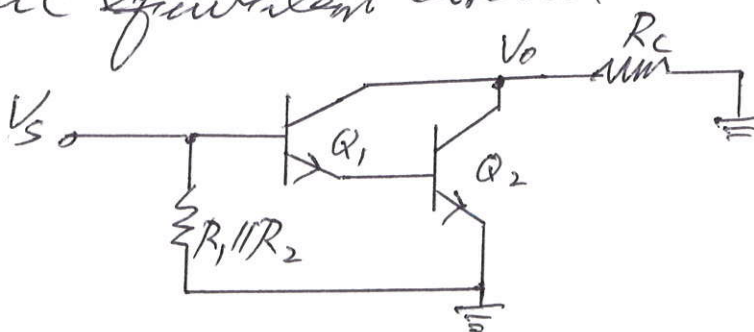

# ac equivalent circuit in detail

6.78 (b)

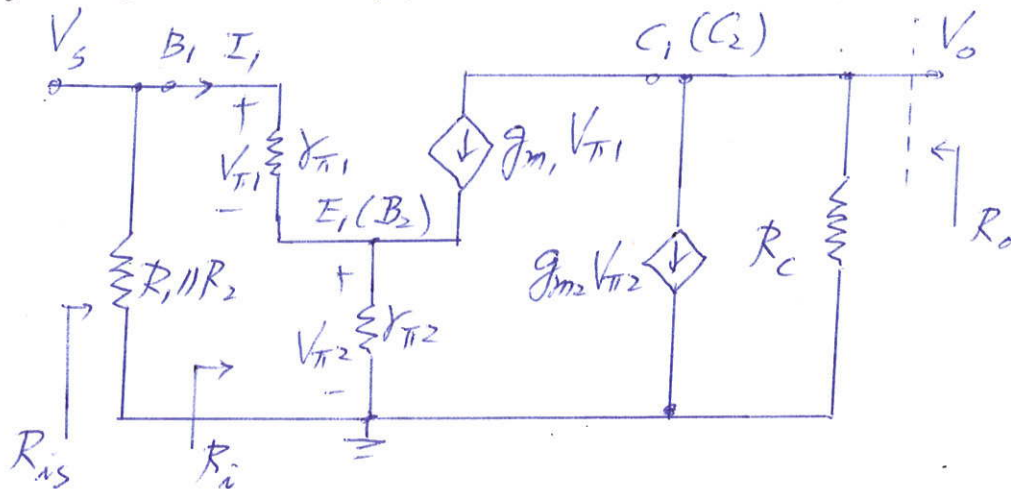

$$r_{\pi 1} = 195.3 \text{ k}\Omega$$

$$r_{\pi 2} = 1.938 \text{ k}\Omega$$

$$\begin{cases} V_o = -(g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2}) \times R_C = -1.126 V_{\pi 1} - 113.52 V_{\pi 2} \\ V_s = V_{\pi 1} + V_{\pi 2} \\ V_{\pi 2} = \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} \right) \times r_{\pi 2} = 0.01 V_{\pi 1} + 0.99 V_{\pi 1} \end{cases}$$

$$\therefore V_{\pi 2} \approx V_{\pi 1}, \quad V_s \approx 2 V_{\pi 1}$$


$$\therefore V_o \approx (-1.126 - 113.52) \times \frac{V_s}{2}$$

$$\frac{V_o}{V_s} \approx -57.3$$

$$R_i = \frac{V_s}{I_1} = \frac{V_s}{V_{\pi 1} / r_{\pi 1}} = \frac{V_s}{V_{\pi 1}} \times r_{\pi 1} \approx 2 r_{\pi 1} = 330 \text{ k}\Omega$$

$$R_{is} = R_1 \parallel R_2 \parallel R_i = \underline{\underline{71.3 \text{ k}\Omega}}$$

Output resistance

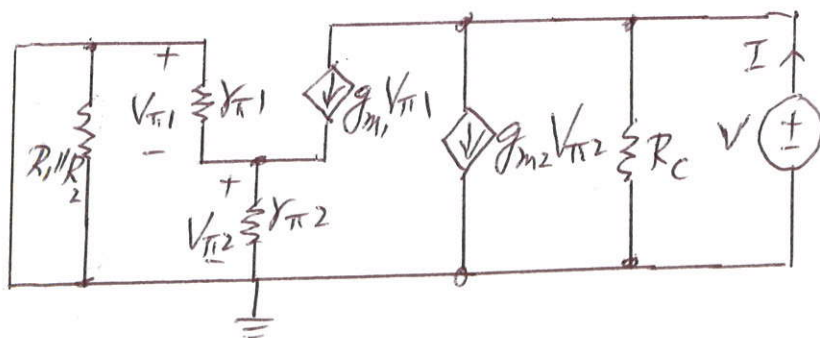

$$\begin{cases} V_{\pi 1} + V_{\pi 2} = 0 \\ V_{\pi 2} = \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} \right) r_{\pi 2} \end{cases}$$

$$V_{\pi 1} = V_{\pi 2} = 0$$

$$\therefore R_o = \frac{V}{I} = R_C = \underline{\underline{2.2 \text{ k}\Omega}}$$