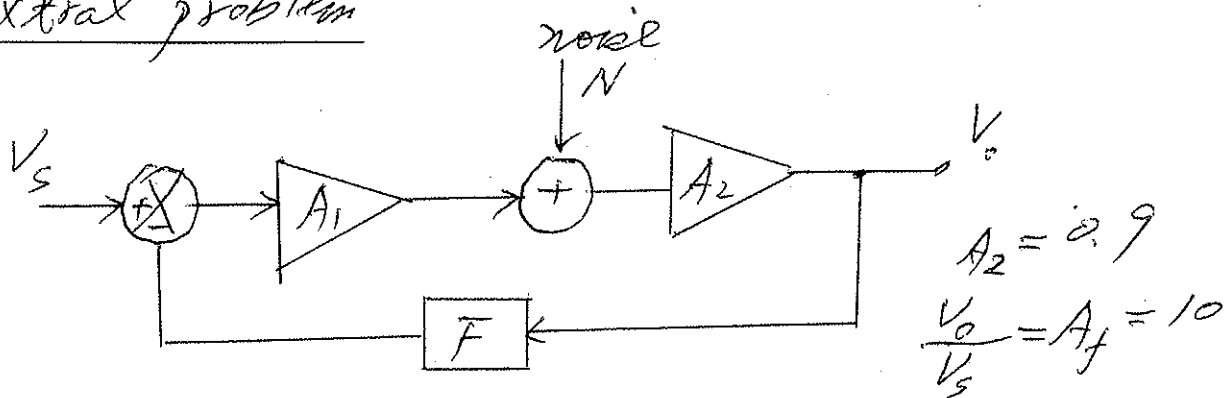


# EECE-315 Exercise #7 Solutions

## Extra problem



$$V_o = [(V_s - FV_o)A_1 + N]A_2$$

$$V_o = (A_1V_s - A_1FV_o + N)A_2 = A_1A_2V_s - A_1A_2FV_o + NA_2$$

$$(1 + A_1A_2F)V_o = A_1A_2V_s + NA_2$$



$$V_o = \left( \frac{A_1A_2}{1 + A_1A_2F} \right) V_s + \left( \frac{A_2}{1 + A_1A_2F} \right) N$$

$\frac{A_1A_2}{1 + A_1A_2F} = 10$  and output ripple noise =  $\frac{A_2}{1 + A_1A_2F} N$

(a)  $A_1 = 100, F = 0.0889$  , (b)  $A_1 = 1000, F = 0.0989$

(c)  $A_1 = 10000, F = 0.09989$

12.15

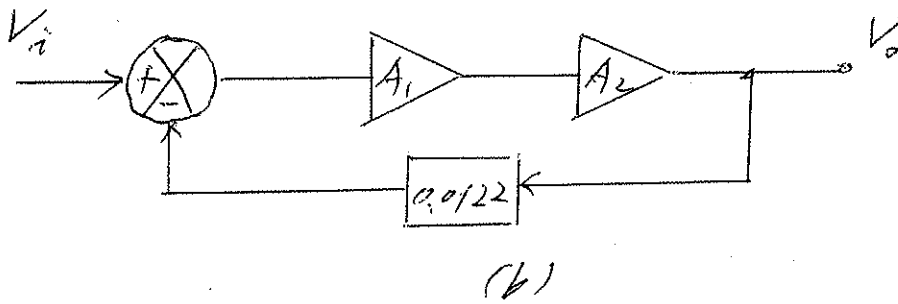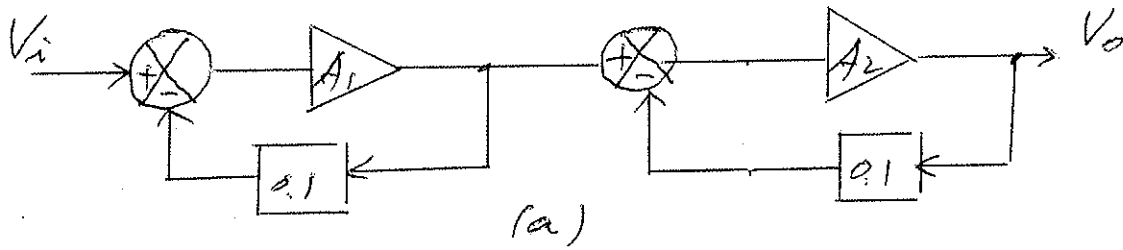

$$(a) \quad \frac{V_o}{V_i} = \frac{A_1}{1 + \beta_1 A_1} \times \frac{A_2}{1 + \beta_2 A_2} = \begin{cases} 81 & \text{for low input} \\ 73.47 & \text{for high input} \end{cases}$$


$$(b) \quad \frac{V_o}{V_i} = \frac{A_1 A_2}{1 + \beta A_1 A_2} = \begin{cases} 81.14 & \text{for low input} \\ 80.14 & \text{for high input} \end{cases}$$

Circuit (b) will result in less distortion.

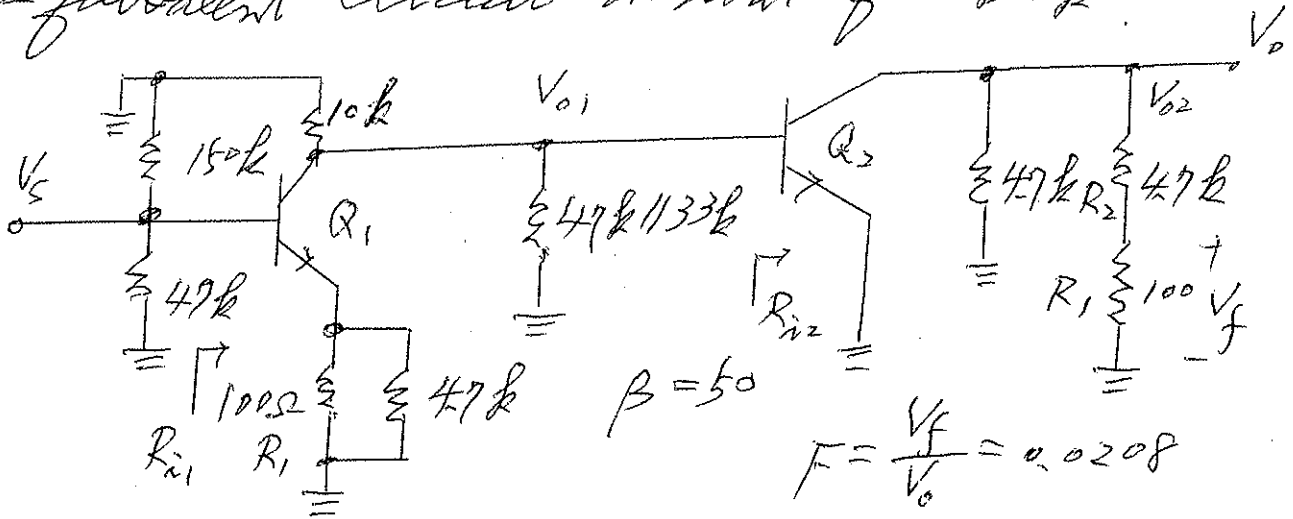12.42

This is a voltage amplifier.

Equivalent circuit without feedback (A-circuit)



From the dc analysis,  $I_{CQ1} = 0.935 \text{ mA}$

$$I_{CQ2} = 1.85 \text{ mA}$$

$$g_{m1} = 37.4 \text{ mA/V}, \quad r_{\pi 1} = \frac{\beta}{g_{m1}} = 1.34 \text{ k}\Omega$$

$$g_{m2} = 74 \text{ mA/V}, \quad r_{\pi 2} = \frac{\beta}{g_{m2}} = 0.676 \text{ k}\Omega$$

$$R_{i2} = r_{\pi 2}, \quad R_{i1} = r_{\pi 1} + (1 + \beta_1)(100 \parallel 4700)$$

$$\frac{V_{o1}}{V_s} = \frac{\beta(10 \parallel 47 \parallel 33 \parallel R_{i2})}{(\beta + 1)(0.1 \parallel 47) + r_{\pi 1}} = -4.84$$

$$\frac{V_{o2}}{V_{o1}} = \frac{V_o}{V_{o1}} = -g_{m2} \times (47 \parallel 4.8) = -175.7$$

$$A = \frac{V_o}{V_s} = 850.4$$

$$A_{Vf} = \frac{V_o}{V_s} \text{ (original circuit)} = \frac{A}{1 + AF} = \underline{\underline{45.5}}$$

12.51 This is a current amplifier.

(a) Do dc analysis  $\beta = 120$


$$I_{C1} = 1.75 \text{ mA}, \quad I_{C2} = 0.50 \text{ mA}$$

$$g_{m1} = 70 \text{ mA/V}, \quad g_{m2} = 20 \text{ mA/V}$$

$$r_{\pi 1} = 1.714 \text{ k}\Omega, \quad r_{\pi 2} = 6 \text{ k}\Omega$$

(b)

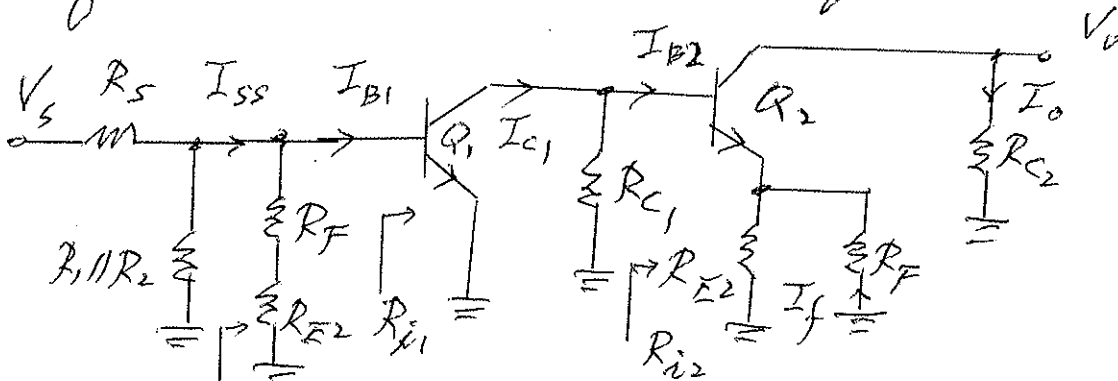Equivalent circuit without feedback (A-circuit)



$$F = \frac{I_f}{I_o} \approx \frac{R_{E2}}{R_{E2} + R_F} = \underline{0.871}$$

$$A = \frac{I_o}{I_{SS}} = \frac{I_o}{I_{B2}} \times \frac{I_{B2}}{I_{C1}} \times \frac{I_{C1}}{I_{B1}} \times \frac{I_{B1}}{I_{SS}}$$

$$R_{i1} = r_{\pi 1}, \quad R_{i2} = r_{\pi 2} + (1 + \beta) \times (R_{E2} \parallel R_F)$$

$$R_{i1} = 1.714 \text{ k}\Omega, \quad R_{i2} = 132.46 \text{ k}\Omega, \quad R_i = (R_F + R_{E2}) \parallel R_{i1} = 1.447 \text{ k}\Omega$$

$$\frac{I_o}{I_{B2}} = -\beta = -120, \quad \frac{I_{B2}}{I_{C1}} = \frac{R_{C1}}{R_{C1} + R_{i2}} = 0.0221$$


$$\frac{I_{C1}}{I_{B1}} = -\beta = -120, \quad \frac{I_{B1}}{I_{SS}} = \frac{R_F + R_{E2}}{R_F + R_{E2} + R_{i1}} = 0.844$$

12.51

$$A = \frac{I_o}{I_{SS}} = \underline{268.6}$$

$$1 + AF = 235$$

Original circuit

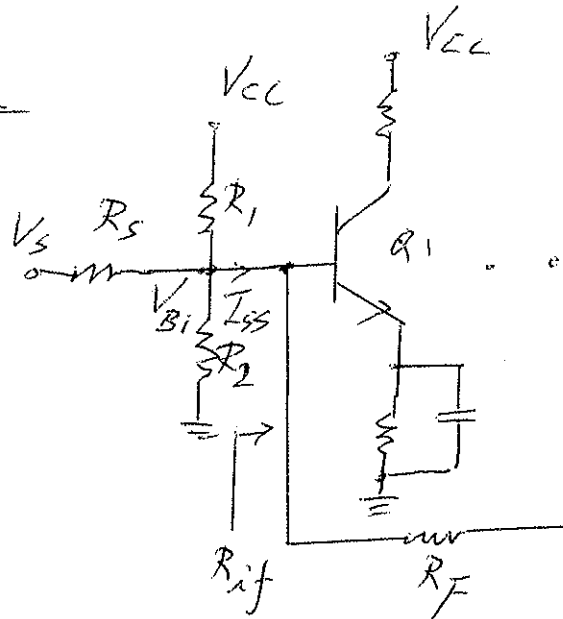

$$\frac{I_o}{I_{SS}} = A_f = \frac{A}{1 + FA}$$

$$\frac{I_o}{I_{SS}} = 1.143$$

$$R_{if} = \frac{R_i}{1 + FA} = 5.88 \Omega$$

$$V_{B1} = I_{SS} \times R_{if} = V_S \times \frac{R_1 \parallel R_2 \parallel R_{if}}{R_S + R_1 \parallel R_2 \parallel R_{if}} = 0.0097 V_S$$

$$\frac{V_o}{V_S} = \frac{I_o \times R_{C2}}{I_{SS} \times R_{if} / 0.0097} = A_f \times \frac{0.0097 \times R_{C2}}{R_{if}}$$

$$\frac{V_o}{V_S} = \underline{7.54}$$


12.57 This is a transconductance amplifier.

$$I_{C1} = 0.5 \text{ mA}, \quad g_{m1} = 20 \text{ mA/V}, \quad r_{\pi1} = 6 \text{ k}\Omega$$

$$I_{C2} = 1 \text{ mA}, \quad g_{m2} = 40 \text{ mA/V}, \quad r_{\pi2} = 3 \text{ k}\Omega$$

$$I_{C3} = 2 \text{ mA}, \quad g_{m3} = 80 \text{ mA/V}, \quad r_{\pi3} = 1.5 \text{ k}\Omega$$

A - circuit

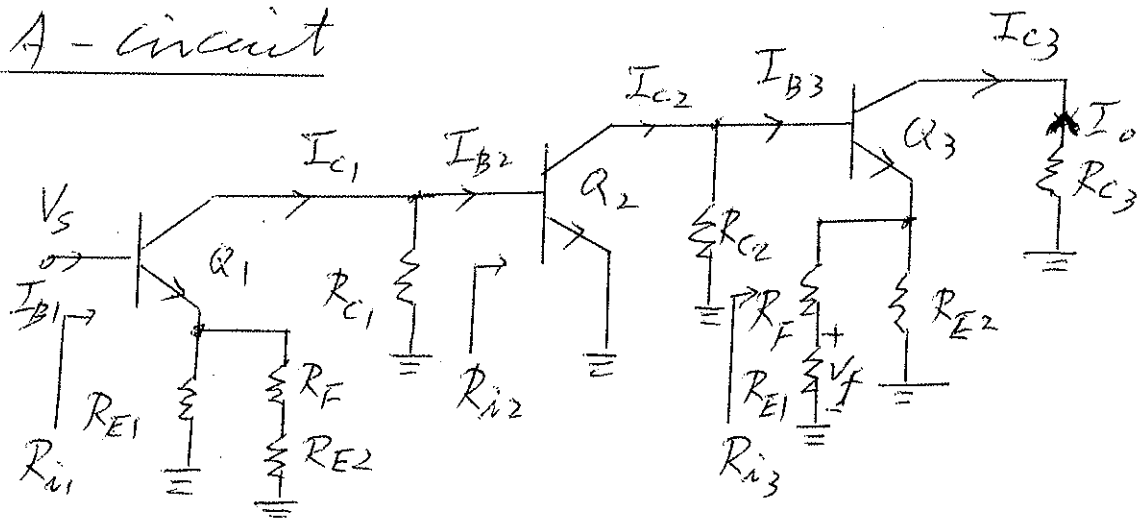

$$F = \frac{V_f}{I_{C3}} \approx - \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} = -0.01 \text{ kV/A} = -10 \text{ V/A}$$

$$A = \frac{I_{C3}}{V_s}, \quad R_{i3} = r_{\pi3} + (120+1) \times [(R_F + R_{E1}) \parallel R_{E2}] = 12.39 \text{ k}\Omega$$

$$R_{i2} = r_{\pi2} = 3 \text{ k}\Omega, \quad R_{i1} = r_{\pi1} + 121 \times [R_{E1} \parallel (R_F + R_{E2})]$$

$$\frac{I_{C3}}{I_{B3}} = -\beta = -120, \quad R_{i1} = 1689 \text{ k}\Omega$$

$$\frac{I_{C1}}{I_{B1}} = -\beta = -120, \quad \frac{I_{C2}}{I_{B2}} = -120$$

$$\frac{I_{B3}}{I_{C2}} = \frac{R_{C2}}{R_{C2} + R_{i3}} = 0.139, \quad \frac{I_{B2}}{I_{C1}} = \frac{R_{C1}}{R_{C1} + R_{i2}} = 0.625$$

$$12.57 \quad \frac{I_{C3}}{I_{B1}} = \frac{I_{C3}}{I_{B3}} \times \frac{I_{B3}}{I_{C2}} \times \frac{I_{C2}}{I_{B2}} \times \frac{I_{B2}}{I_{C1}} \times \frac{I_{C1}}{I_{B1}} = -150120$$

$$V_S = I_{B1} \times R_{in1} = 16.89 \times I_{B1} \times 10^3$$

$$\therefore A = \frac{I_{C3}}{V_S} = \frac{I_{C3}}{I_{B1}} \times \frac{I_{B1}}{V_S} = -8.888$$

$$AF + 1 = 89.88$$


---

Original circuit

$$A_f = \frac{I_{C3}}{V_S} = \frac{A}{1 + AF} = -0.0989$$

$$\therefore \frac{I_o}{V_S} = \frac{-I_{C3}}{V_S} = 0.0989 \text{ A/V} = \underline{\underline{98.9 \text{ mA/V}}}$$


12.61 This is a transresistance amplifier.

$$\beta = 80, V_{EB} = 0.7 \text{ V}, V_A = 100 \text{ V}.$$

DC analysis :  $I_{CQ} = 2.448 \text{ mA}$   
 $V_{ECQ} = 1.31 \text{ V}$

$$g_m = \frac{I_{CQ}}{0.025} = 97.92 \text{ mA/V}, r_{\pi} = \frac{80}{g_m} = 817 \Omega, r_o = \frac{V_A}{I_{CQ}} = 40.85 \text{ k}\Omega$$

A-circuit

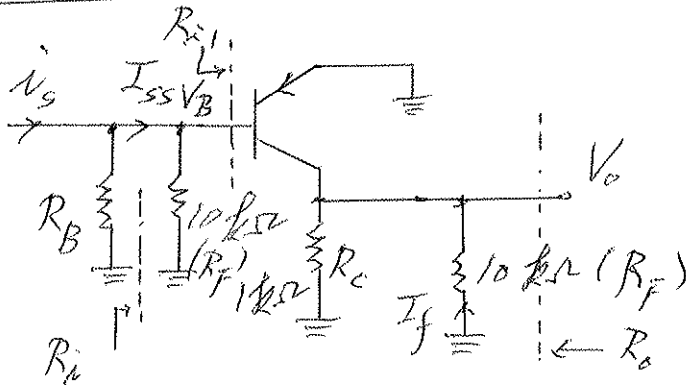

$$F = \frac{I_f}{V_o} = -\frac{1}{R_F} = -10^{-4} \text{ A/V}$$

$$A = \frac{V_o}{I_{ss}}, R_{in} = r_{\pi} = 0.817 \text{ k}\Omega$$

$$\frac{V_o}{V_B} = -g_m (R_C \parallel R_F \parallel r_o)$$

$$\frac{V_o}{V_B} = -g_m \times 0.889 = -87.1$$

$$V_B = I_{ss} \times (10 \parallel R_{in}) = 0.755 I_{ss}$$

$$\therefore A = \frac{V_o}{I_{ss}} = \frac{V_o}{V_B} \times \frac{V_B}{I_{ss}} = \underline{\underline{-67.76 \text{ kV/A}}}$$

$$1 + AF = 2.576, R_i = R_{in} \parallel R_F = 0.755 \text{ k}\Omega$$

$$R_o = R_C \parallel R_F \parallel r_o = 0.889 \text{ k}\Omega$$

Original circuit:  $R_{of} = \frac{R_o}{1 + AF} = \underline{\underline{117.3 \Omega}}$

$$R_{if} = \frac{R_i}{1 + AF} \parallel R_B = 0.0997 \parallel 100 = \underline{\underline{99.6 \Omega}}$$

$$\frac{V_o}{v_s} = \frac{V_o}{I_{ss}} \times \frac{I_{ss}}{i_s} = (A_f) \times \frac{R_B}{R_B + \frac{R_i}{1 + AF}} = \frac{-67.76}{2.576} \times \frac{100}{100 + 0.0997}$$

$$\frac{V_o}{v_s} = \underline{\underline{-8.944 \text{ kV/A}}}$$