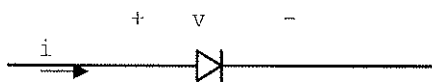


### Voltage-current relationship of a p-n junction diode



$$i = I_s (e^{qv/nkT} - 1)$$

$$V_T = kT/q$$

$I_s$  saturation current (reverse saturation),  $I_s > 0$

$k$  Boltzmann's constant;  $k = 1.38 \times 10^{-23}$  joules/K =  $8.62 \times 10^{-5}$  eV/K

$T$  Absolute temperature = 273 + temperature in °C

$q$   $1.60 \times 10^{-19}$  coulombs = 1 e

$n$  an adjusting factor (emission coefficient),  $1 \leq n \leq 2$

$V_T$  volt-equivalent of temperature, thermal voltage  
 =  $T/116000$  volts  
 $\cong 25$  mV at room temperature (20 °C,  $T = 293$  K)  
 $\cong 26$  mV at temperature 25 °C



When  $v >$  the cut-in voltage,  $i \cong I_s e^{qv/nkT} = I_s \exp(qv/kT)$ .

Cut-in voltage    0.2 to 0.3 volts for a germanium diode  
                       0.5 to 0.6 volts for a silicon diode



$$I_s(T) = I_s(T_1) \times 2^{(T-T_1)/10} \text{ A}$$

$$\frac{dv}{dT} \cong -2.2 \text{ mV}/^\circ\text{C} \quad (\cong -2 \text{ mV}/^\circ\text{C})$$

# Modeling the diode

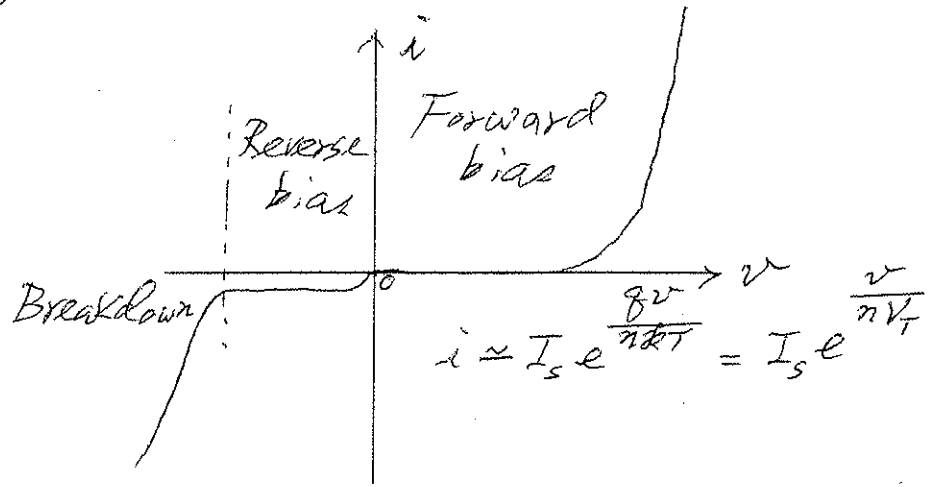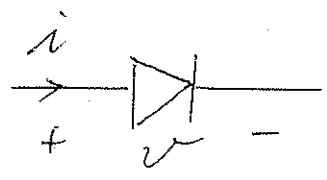
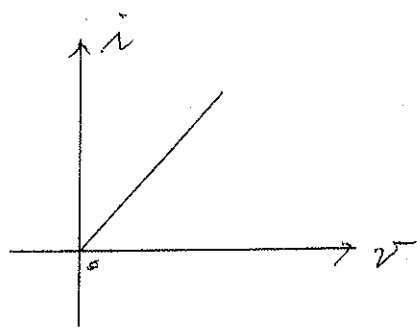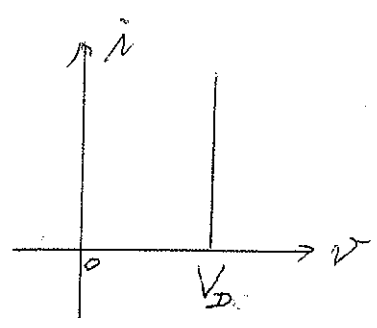
## Forward-biased diode piecewise linear characteristics






Small signal model


$$\frac{di}{dv} \approx I_s \cdot \frac{1}{nV_T} e^{\frac{v}{nV_T}}$$

$$r_d \approx \frac{nV_T}{i}$$

Incremental resistance

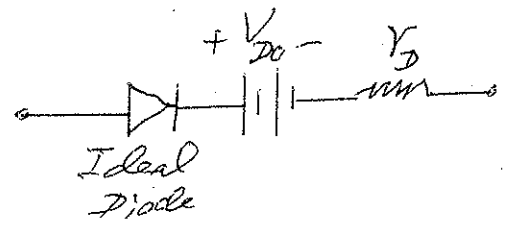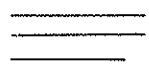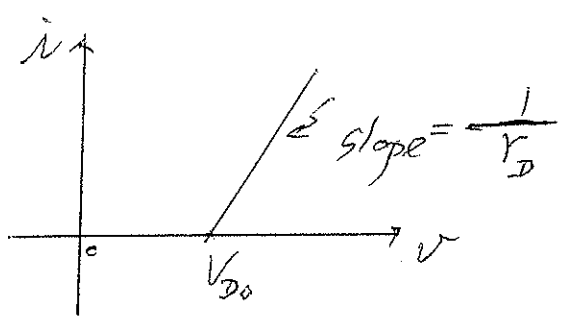


## Ideal diode characteristic

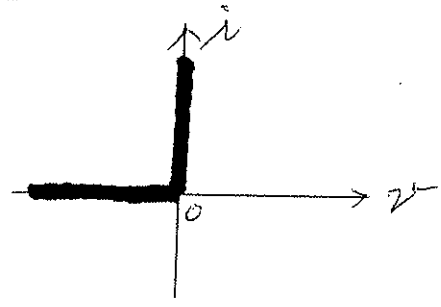

$$v < 0 \Rightarrow i = 0$$

$$i > 0 \Rightarrow v = 0$$

### Zener Diode (Breakdown diode)

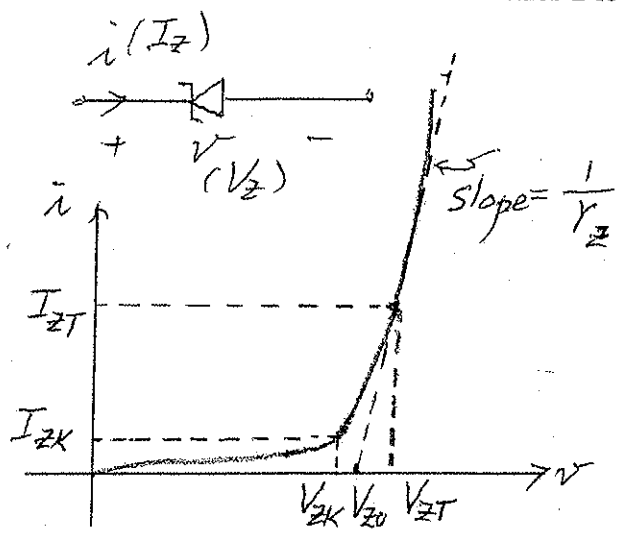

dynamic resistance (incremental resistance)

$$r_z = \frac{\Delta V_Z}{\Delta I_Z}$$

$$\Delta V_Z = r_z \cdot \Delta I_Z$$

Ideally,  $r_z = 0, \Delta V_Z = 0$   
 $V_Z$  is a constant.

Typically,  $10 \text{ V} < V_Z < 6 \text{ V}$ ;  $r_z \approx$  a few ohms  
 Otherwise,  $r_z \approx$  hundreds of ohms



$V_Z < 5 \text{ V}$ : negative temperature coefficient (TC)  
 Higher  $V_Z$ : positive temperature coefficient

- $I_{ZK}$  knee current (minimum current) for a good regulation
- $V_{ZK}$  breakdown voltage (Zener voltage) at  $I_{ZK}$
- $I_{ZT}$  test current
- $V_{ZT}$  Zener voltage at  $I_{ZT}$
- $r_z$  dynamic resistance at  $I_{ZT}$  and  $V_{ZT}$
- $P_Z$  Power rating (Watts);  $P_Z = I_{ZT} V_{ZT}$





Equivalent circuit model of a Zener diode

$$V = V_{Z0} + r_z i$$

or  $V_Z = V_{Z0} + r_z \cdot I_Z$

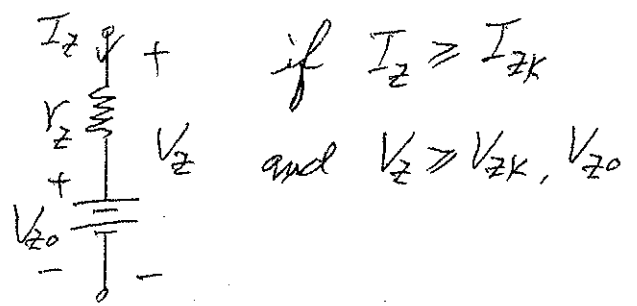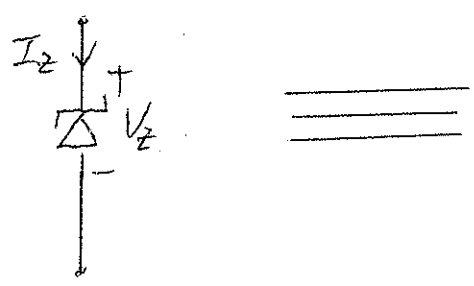

# Bipolar Junction Transistor (BJT)

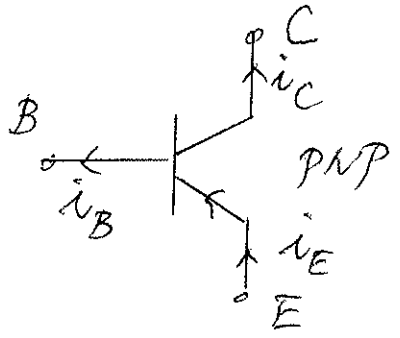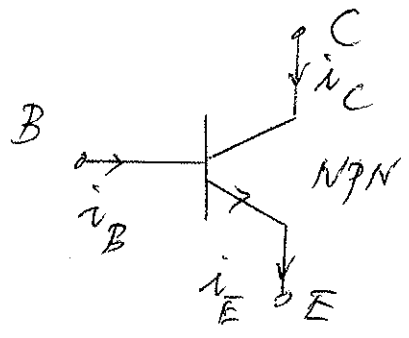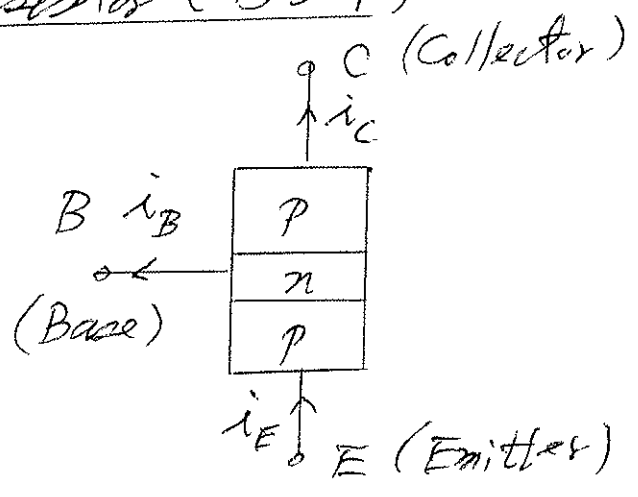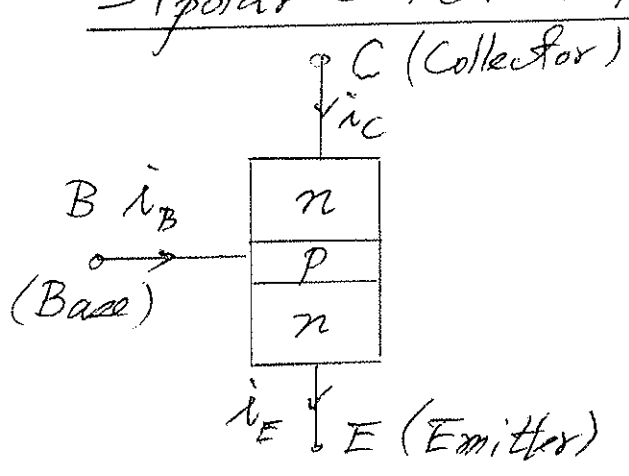

$$i_B + i_C = i_E$$

## Four Regions of Operations

- ① Cutoff — Both junctions reverse biased.
- ② Active — EB forward biased  
(Normal, Forward) CB reverse biased
- ③ Saturation — Both junctions forward biased
- ④ Reverse active — EB reverse biased  
(Inverted active) CB forward biased

## Cutoff Region

$$I_E = 0, \quad I_C = I_{CO} \text{ (Reverse leakage current)}$$

$$I_B = -I_C = I_{CBO} \text{ (Very small)}$$

$$I_B \approx 0, \quad I_C = 0 \text{ and } I_E = 0$$

## Active Region

$$|V_{BE}| = 0.7 \text{ V}, \quad I_B > 0$$

$$I_C = \beta I_B, \quad I_E = (\beta + 1) I_B$$

## Saturation Region

$$V_{CE} = 0.2 \text{ to } 0.4 \text{ V for NPN BJT}$$

$$V_{EC} = 0.2 \text{ to } 0.4 \text{ V for PNP BJT}$$

$$|V_{BE}| = 0.75 \text{ V to } 0.8 \text{ V}$$

$$I_C \leq \beta I_B$$

$$\frac{I_C}{I_B} = \beta_{\text{forced}} \leq \beta$$

$$\frac{\beta}{\beta_{\text{forced}}} = \text{overdrive factor}$$