
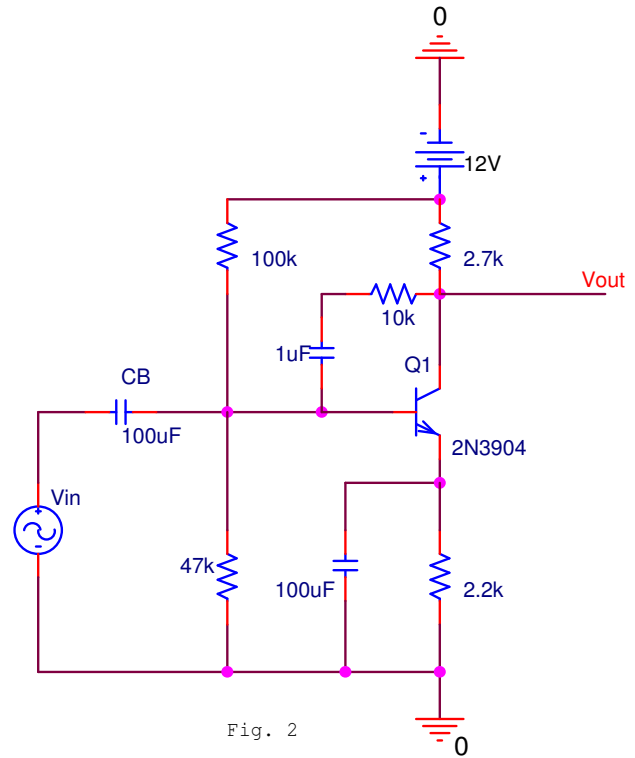


EECE-315 Prelab 13

1. Refer to the circuit shown in Fig. 1. The output current is the current leaves the collector. Calculate the open-loop and closed-loop transconductance midband gains. Also calculate the lower -3 dB cutoff frequencies with the feedback loop open and closed.

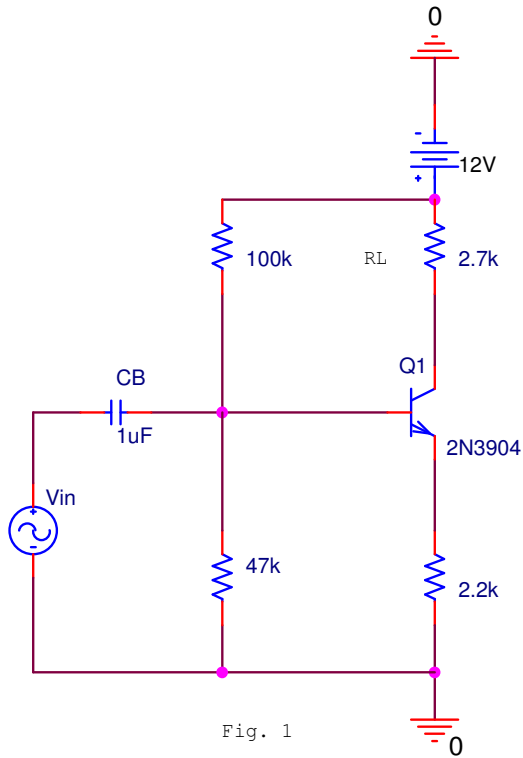2. Refer to the circuit shown in Fig. 2. Calculate the open-loop and closed-loop transresistance midband gains.



EECE-315 Lab 13

1. Build the circuit shown in Fig. 1 on the prelab. Measure the voltage gain (closed-loop gain) at 1 kHz, and determine the lower – 3dB cutoff frequency.
2. Connect an emitter bypass capacitor, C_E , of at least 1000 μF across R_E . Measure the voltage gain (open-loop gain) at 1 kHz, and determine the lower – 3 dB cutoff frequency.
3. Compare the open-loop and closed-loop transconductance gains you measured to the theoretically calculated values.
4. Compare the lower –3 dB cutoff frequencies of this amplifier with the loop closed (without C_E) and open (with C_E).
4. Build the circuit shown in Fig. 2 on the prelab. Insert a decade resistance box (~ 10 kohms) between the input voltage source, V_{in} , and the input blocking capacitor, C_B . Use a differential mode to display the voltage across the decade resistance box. Dividing the voltage by the resistance gives the input current of the feedback amplifier. Measure the transresistance gain (closed-loop) at 1 kHz.
5. Remove the 10 $k\Omega$ from the circuit. Measure the transresistance gain (open-loop) at 1 kHz.
6. Compare the open-loop and closed-loop transresistance gains you measured to the theoretically calculated values.