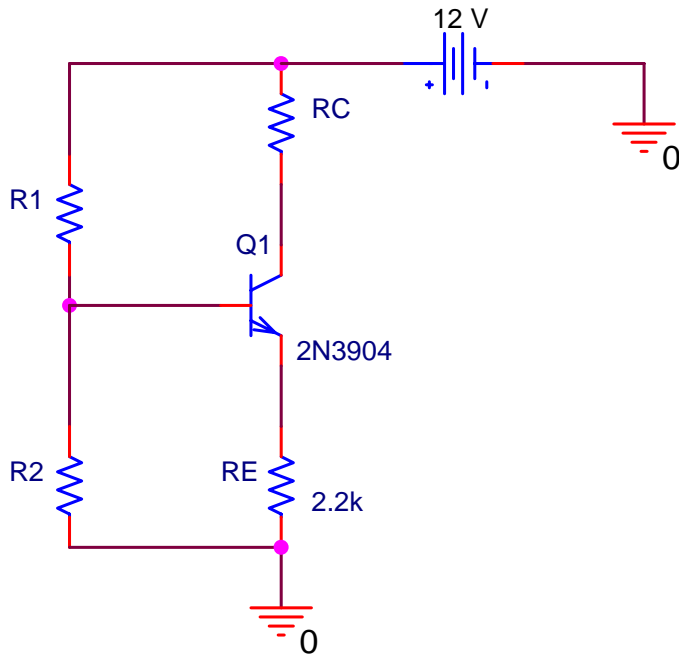


EECE-315 Prelab 5

1. Assuming $\beta = 100$, design a bias circuit to give a nominal $I_{CQ} = 2 \text{ mA}$ with a supply voltage of 12 V . Assume the BJT is biased in its active region and the emitter resistance is $2.2 \text{ k}\Omega$.
2. Calculate the largest value of collector resistance, $R_{C,\text{max}}$, that will allow the transistor to remain in active region. Assume $V_{CE(\text{min})} = 0.4 \text{ V}$.



EECE-315 Lab 5

1. Let $R_C = 0 \Omega$ (short circuit). Build the circuit that you designed in the prelab. Measure the quiescent collector current. Correlate your measurement to the theoretically value given in the prelab.
 2. Use a Tektronix curve tracer to display and plot the i-v family curves of your 2N3904 transistor. Scale the curves to display from the origin to the maximum v_{CE} ($I_C = 0$) and the maximum i_C ($V_{CE} = 0$).
 3. From the i-v curves, determine the values of dc β and ac β . Here is the procedure to determine them:
 - (a) Draw the dc load line of your circuit on the plotted i-v curves.
 - (b) Mark the Q-point you measured on the load line. Divide I_{CQ} by I_{BQ} to get β_{dc} .
 - (c) Draw a vertical line through the Q-point and find the values of I_C where it intersects with the curves either above or below the Q-point.
 - (d) Subtract those two values of I_C to call it ΔI_C .
 - (e) Divide ΔI_C by ΔI_B to get β_{ac} .
- NOTE: You may need to re-run the curve tracer to get a plot over proper ranges of v_{CE} and i_C .
4. Calculate the I_{CQ} using the measured β_{dc} .
 5. You will be given two other transistors. Measure their β_{dc} on the curve tracer. DO NOT make hard copies of the displayed curves. Insert each of them into your circuit and record I_{CQ} and V_{CEQ} . Discuss your results.
 6. Place the 2N3904 transistor in the circuit and increase R_C until the collector-emitter voltage drops to 0.4 V. Call this $R_{C,max}$. Measure the I_{CQ} .
 7. Repeat the calculation done in part 2 of the prelab using the measured I_{CQ} in part 1 of the lab. Compare the result of this calculation to $R_{C,max}$.
 8. Plot the dc load lines for $R_C = 0$ and $R_{C,max}$ on your hard copy of the i-v curves. Mark the Q-point in each case.